

第九次普物作業 E94086107 張明聰


17.

(a) $B = \mu_0 n I = \mu_0 \frac{400}{0.25} \cdot 80 = 0.16 \text{ T}$ (b) $U_B = \frac{1}{2\mu_0} B^2 = 10313.64 \text{ J/m}^3$

(c) $E = \frac{1}{2} L I^2 = \frac{1}{2} \frac{B^2}{\mu_0} A l = \frac{1}{2} \frac{0.16^2}{\mu_0} \times 0.5 \times 10^{-4} \times 0.25 = 0.129 \text{ J}$

(d) $E = \frac{1}{2} L I^2$ $L = 4.03 \times 10^{-5} \text{ H}$

23.

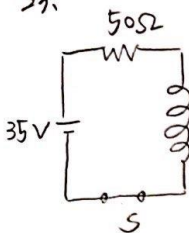

(a) $V - IR - L \frac{dI}{dt} = 0$

maximum when $t=0$ $I = \frac{V}{R} = I_0 = 0.7 \text{ A}$

now $I = \frac{1}{2} I_0$, find t

$\int_0^I \frac{dI}{V - IR} = \int_0^t \frac{dt}{L}$

$I = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$


$\frac{1}{2} \frac{V}{R} = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$ $e^{-\frac{R}{L}t} = \frac{1}{2}$

$t = 1.73 \times 10^{-5} \text{ s}$

(b) $E = \frac{1}{2} L I_{\text{max}}^2 = E_{\text{max}}$ now $E = \frac{1}{2} E_{\text{max}}$ $I = \frac{1}{\sqrt{2}} I_{\text{max}}$ $\frac{1}{\sqrt{2}} \frac{V}{R} = \frac{V}{R} (1 - e^{-\frac{R}{L}t})$ $t = 3.07 \times 10^{-5} \text{ s}$

35

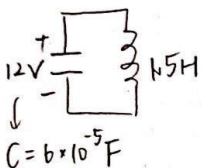(a) for a L-C circuit $\omega_0 = \frac{1}{\sqrt{LC}} = 105.41 \text{ rad/s}$ $T = \frac{2\pi}{\omega} = 5.96 \times 10^{-2} \text{ s}$



(b) initial charge: $V_0 = \frac{Q_0}{C}$ $12 = \frac{Q_0}{6 \times 10^{-5}}$ $Q_0 = 7.2 \times 10^{-4} \text{ C}$

(c) $E_C = \frac{1}{2} C V^2$ $E_{C \text{ initial}} = \frac{1}{2} C V_0^2 = 4.32 \times 10^{-3} \text{ J}$


(d) $q(t) = Q_0 \cos(\omega_0 t + \phi)$ $q(0.023) = -5.4 \times 10^{-4} \text{ C}$ negative signed means capacitor is fully discharged, then it charged by the current in the inductor.
($q(0) = Q_0$, $\phi = 0$.)

(e) $I(t) = \omega_0 Q_0 \sin(\omega_0 t + \phi)$ $I(0.023) = 4.99 \times 10^{-2} \text{ A}$ so direction is the same as beginning

(f) $E_C = \frac{Q_0^2}{2C} \cos^2(\omega_0 t + \phi)$ $E_C(0.023) = 2.45 \times 10^{-3} \text{ J}$ $E_L = E_C - E_C = 1.87 \times 10^{-3} \text{ J}$

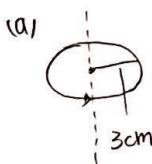43.

$i(t) = I_0 \sin(2\pi f t)$ $I_0 = 1.2 \text{ A}$ $f = 69 \text{ Hz}$ $\text{radius} = 3 \text{ cm}$



$\Phi_B = B_{\text{center}} \cdot A_{\text{coil}}$ $A_{\text{coil}} = R^2 \pi$

$N \frac{d\Phi_B}{dt} = L \frac{dI}{dt}$ $\Phi_B = \frac{\mu_0 I R}{2} i(t)$



$B_{\text{center}} = \frac{\mu_0 I}{2R}$ $N \frac{d\Phi_B}{dt} = L \frac{dI}{dt}$

$N \cdot \frac{\mu_0 I R}{2} \frac{di(t)}{dt} = \frac{di(t)}{dt} L$

$L = 1 \cdot \frac{\mu_0 \pi R \cdot 0.3}{2} = 59.2 \times 10^{-9} \text{ H}$

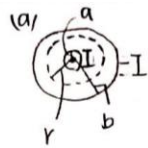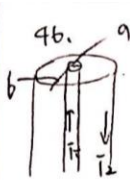(b) $\mathcal{E}_L = L \frac{dI}{dt} = 59.2 \times 10^{-9} \times \frac{di(t)}{dt} = 59.2 \times 10^{-9} \times I_0 \cdot 2\pi f \times \cos(2\pi f t)$


maximum $\mathcal{E}_L = \text{when } \sin(2\pi f t) = 1$, $\mathcal{E}_{L \text{ max}} = 2.68 \times 10^{-5} \text{ V}$



$$\oint \mathbf{B} \cdot d\mathbf{l} = \mu_0 I$$

$$B \cdot 2\pi r = \mu_0 I$$

$$B = \frac{\mu_0 I}{2\pi r}$$

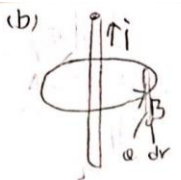

$$\Phi_B = B \cdot A$$


$$d\Phi_B = B \cdot dA$$

$$= \frac{\mu_0 I}{2\pi r} \times dA$$

$$(c) \Phi_B = \int d\Phi_B = \int_a^b \frac{\mu_0 I}{2\pi r} \cdot 2\pi r \, dr = \frac{\mu_0 I}{2\pi} \int_a^b \frac{dr}{r} = \frac{\mu_0 I}{2\pi} \ln\left(\frac{b}{a}\right)$$

$$(d) L = \frac{N\Phi}{I}, N=1 \quad L = \frac{\mu_0 I}{I} \ln\left(\frac{b}{a}\right) = \frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right)$$
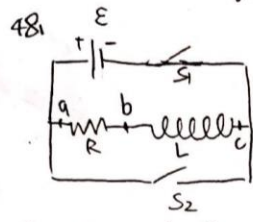
$$(e) U = L \int_0^I i \, di = \frac{1}{2} L I^2 = \frac{1}{2} \frac{\mu_0}{2\pi} \ln\left(\frac{b}{a}\right) \cdot I^2 = \frac{\mu_0 I^2}{4\pi} \ln\left(\frac{b}{a}\right)$$



(a) eq 30.14

$$i = \frac{E}{R} (1 - e^{-\frac{R}{L}t})$$

$$P_R = I_R V_R = I_R \cdot I_R R = I_R^2 R$$

$$I_R = i$$

$$P_R = \left(\frac{E}{R}\right)^2 (1 - e^{-\frac{R}{L}t})^2 R$$

$$= \frac{E^2}{R} (1 - e^{-\frac{R}{L}t})^2$$

$$P_{R \text{ max}} = \frac{E^2}{R}$$

$P_R \text{ max when } t=0$

$t=0$ S_1 closed S_2 open

$$(b) \text{ eq 30.15 } \frac{di}{dt} = \frac{E}{L} e^{-\frac{R}{L}t} \quad P_L = i V_L = i L \frac{di}{dt} = \frac{E}{R} (1 - e^{-\frac{R}{L}t}) \cdot L \cdot \frac{E}{L} e^{-\frac{R}{L}t} = \frac{E^2}{R} (1 - e^{-\frac{R}{L}t}) (e^{-\frac{R}{L}t})$$

$$(c) t=0, P_L(0) = \frac{E^2}{R} (1 - e^0)(e^0) = 0 \quad t \rightarrow \infty \quad P_L = \frac{E^2}{R} (1 - e^{-\infty})(e^{-\infty}) = 0 \quad \text{both } 0$$

$$(d) P_L \text{ Max, } \frac{dP_L}{dt} = \frac{E^2}{R} \frac{d(1 - e^{-\frac{R}{L}t})(e^{-\frac{R}{L}t})}{dt} = \frac{E^2}{R} \frac{d(e^{-\frac{R}{L}t} - e^{-\frac{2R}{L}t})}{dt} = \frac{E^2}{R} \left(-\frac{R}{L} e^{-\frac{R}{L}t} + \frac{2R}{L} e^{-\frac{2R}{L}t}\right)$$


$$\frac{dP_L}{dt} = 0 \quad e^{-\frac{R}{L}t} = \frac{1}{2} \quad t = -\frac{L}{R} \ln\left(\frac{1}{2}\right) \quad \text{when } t = -\frac{L}{R} \ln\left(\frac{1}{2}\right), P_L = \frac{E^2}{R} (1 - e^{\ln\frac{1}{2}})(e^{\ln\frac{1}{2}}) = \frac{E^2}{R} \left(1 - \frac{1}{2}\right)\left(\frac{1}{2}\right) = \frac{0.25 E^2}{R}$$

$P_L \text{ max}$

$$(e) P_E = P_R + P_L = \frac{E^2}{R} (1 - e^{-\frac{R}{L}t})^2 + \frac{E^2}{R} (1 - e^{-\frac{R}{L}t}) (e^{-\frac{R}{L}t}) = \frac{E^2}{R} (1 - e^{-\frac{R}{L}t})$$

$$P_E \text{ max, } 1 - e^{-\frac{R}{L}t} = 1 \quad e^{-\frac{R}{L}t} = 0 \quad t \rightarrow \infty, P_E \text{ max} = \frac{E^2}{R}$$


50.

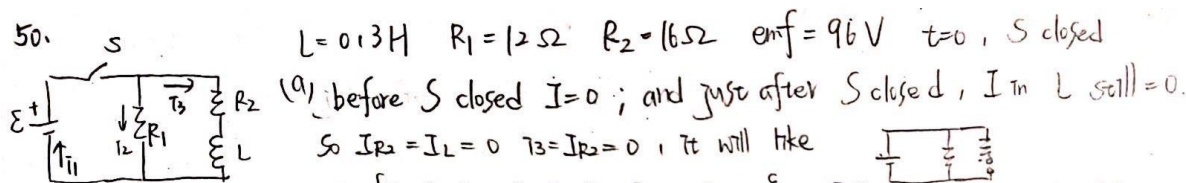

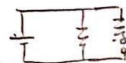(a) before S closed $I = 0$; and just after S closed, I in L still $= 0$.

So $I_{R2} = I_L = 0$ $I_3 = I_{R2} = 0$, it will like


as for i_1, i_2 $I_1 = I_2 + I_3 = I_2$ $I_2 = \frac{\epsilon}{R} = 8 \text{ A}$



$A: I_1 = I_2 = 8 \text{ A}$ $I_3 = 0$

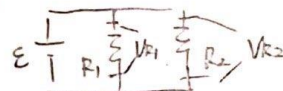
(b) after for a long time, $I_L = 0$, 不會有反應, just like

$I_1 = I_2 + I_3$ $I_2 = \frac{V_{R1}}{R_1}$ $I_3 = \frac{V_{R2}}{R_2}$ $V_{R1} = V_{R2} = \epsilon$



$I_2 = \frac{96}{12} = 8$ $I_3 = \frac{96}{16} = 6$ $I_1 = 8 + 6 = 14 \text{ A}$ $A: I_1 = 14 \text{ A}$ $I_2 = 8 \text{ A}$ $I_3 = 6 \text{ A}$

(c) we can see I_3 as $R-L$ circuit

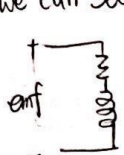

$I_3 = I = \frac{\epsilon}{R} (1 - e^{-\frac{R}{L}t})$


$t \rightarrow \infty$ $I_3 = \frac{\epsilon}{R}$

find t when $I_3 = \frac{1}{2} \frac{\epsilon}{R}$

$\frac{1}{2} \frac{\epsilon}{R} = \frac{\epsilon}{R} (1 - e^{-\frac{R}{L}t})$

$e^{-\frac{R}{L}t} = \frac{1}{2}$ $t = 1.30 \times 10^{-2} \text{ s}$

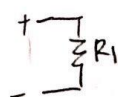
(d) I_2 still 8 A since it is a circuit like this



$I_2 = \frac{\text{emf}}{R_1} = 8 \text{ A}$

$I_1 = I_2 + I_3$, $I_1 = 8 + \frac{1}{2} \cdot 6 = 11 \text{ A}$

61.

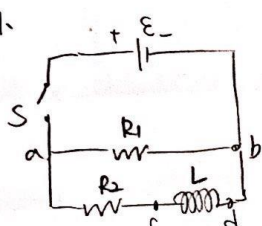

$t=0$, switch is closed

$\epsilon = 60 \text{ V}$ $R_1 = 40 \Omega$ $R_2 = 25 \Omega$ $L = 0.3 \text{ H}$

(a) $V_{ab} = 60 \text{ V}$, since R_1 in parallel ∞ R_2 and L $V_{R1} = V_{R2} + V_L = \epsilon$

(b) point a has higher potential


(c) just after S closed, $I_L = 0$. $\epsilon - I_2 R_2 - V_L = 0$. $\epsilon - 0 - V_L = 0$
($V_L = V_{cd}$)

$V_L = V_{cd} = \epsilon = 60 \text{ V}$

(d) c is higher point. (e) just after switch is closed, $V_{R1} = \epsilon = 60 \text{ V}$

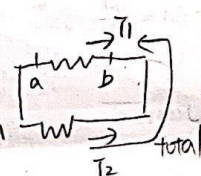
(f) after a long time of closing the switch, the inductor has zero voltage,

and since $I_1 = \frac{60}{40} = 1.5$ $I_2 = \frac{60}{25} = 2.4$, the current will flow in opposite direction through the branch as R_1 . So b has higher potential.




(g) $V_L - I_2 R_2 - I_2 R_1 = 0$ ($V_L = I_2 (R_1 + R_2) = 2.4 (65) = 156 \text{ V}$)

(h)

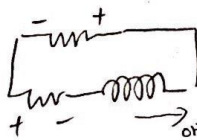

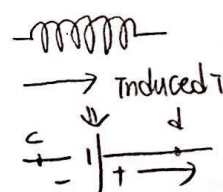I is decreasing, this will induce emf
st this emf produce same direction




\Rightarrow got d has higher pote

補:


$$50. (d) i_2 = \frac{emf}{R_1} = 8A$$

61(h) 最右邊: d has higher potential

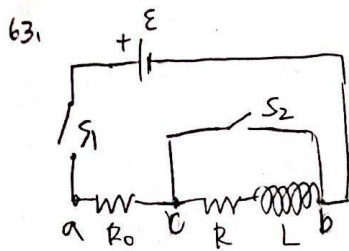


$$\varepsilon = 36V \quad R_0 = 50\Omega \quad R = 150\Omega \quad L = 4H$$

(a)

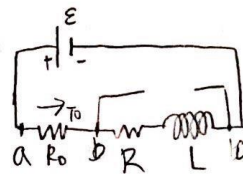

just after switch S_1 closed, $I_L(0^-) = 0$, so $I_L(0^+) = 0$
current can't increase suddenly in inductor
so $I_0 = 0$ (they are series now)
then $V_{ac} = 0$

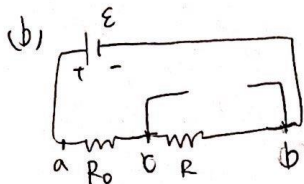Since no voltage drop in R_0 , $V_{cb} = emf = 36V$




$$\Sigma R = R_0 + R = 200\Omega$$

$$V_{ac} = I_0 R_0 = 9V$$

$$I = \frac{\varepsilon}{\Sigma R} = 0.18A$$

$$V_{cb} = I R = 27V$$

$$I_0 = I = 0.18A$$

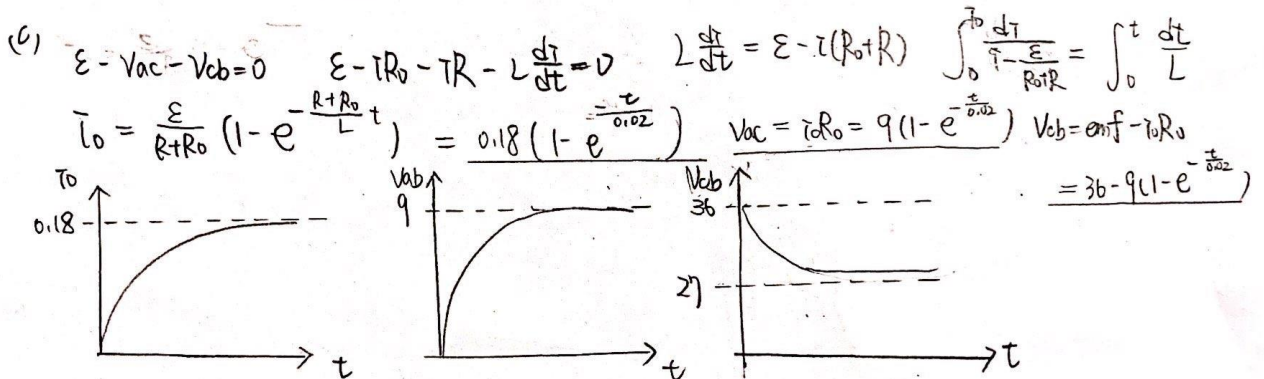

$$63(c) : V_{cb} = 36 - 9(1 - e^{-\frac{t}{0.02}})$$