




成功大學

National Cheng Kung University

Chapter 4

The Processor

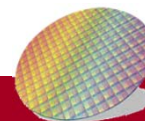

Introduction

- CPU performance factors

- Instruction count

- Determined by ISA and compiler

- CPI and Cycle time

- Determined by CPU hardware

$$\text{CPU Time} = \text{Instruction Count} \times \text{CPI} \times \text{Clock Cycle Time}$$

- We will examine two MIPS implementations

- A simplified version (Single-cycle implementation)

- A more realistic pipelined version


- Multi-cycle version is removed in this version

- Implement simple inst. subset, but shows most aspects

- Memory reference: lw, sw

- Arithmetic/logical: add, sub, and, or, slt

- Control transfer: beq, j

 


Review: MIPS Instruction Set Architecture (ISA)



- Instruction Categories

- Arithmetic
- Load/Store
- Jump and Branch
- Floating Point
 - coprocessor
- Memory Management
- Special

Registers

 


3 Instruction Formats: all 32 bits wide

 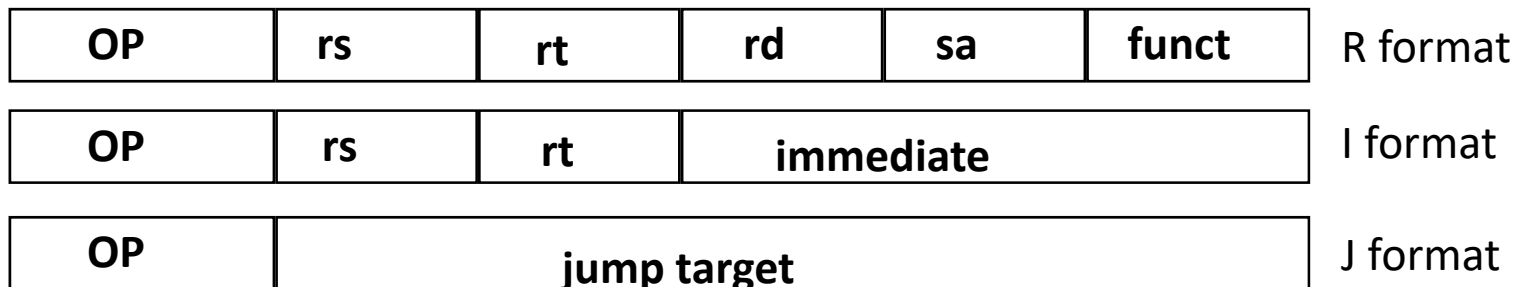



Review: MIPS Register Convention

Name	Register Number	Usage	Preserve on call?
\$zero	0	constant 0 (hardware)	n.a.
\$at	1	reserved for assembler	n.a.
\$v0 - \$v1	2-3	returned values	no
\$a0 - \$a3	4-7	arguments	yes
\$t0 - \$t7	8-15	temporaries	no
\$s0 - \$s7	16-23	saved values	yes
\$t8 - \$t9	24-25	temporaries	no
\$gp	28	global pointer	yes
\$sp	29	stack pointer	yes
\$fp	30	frame pointer	yes
\$ra	31	return addr	yes

 

Instruction Execution

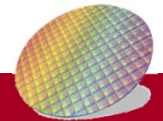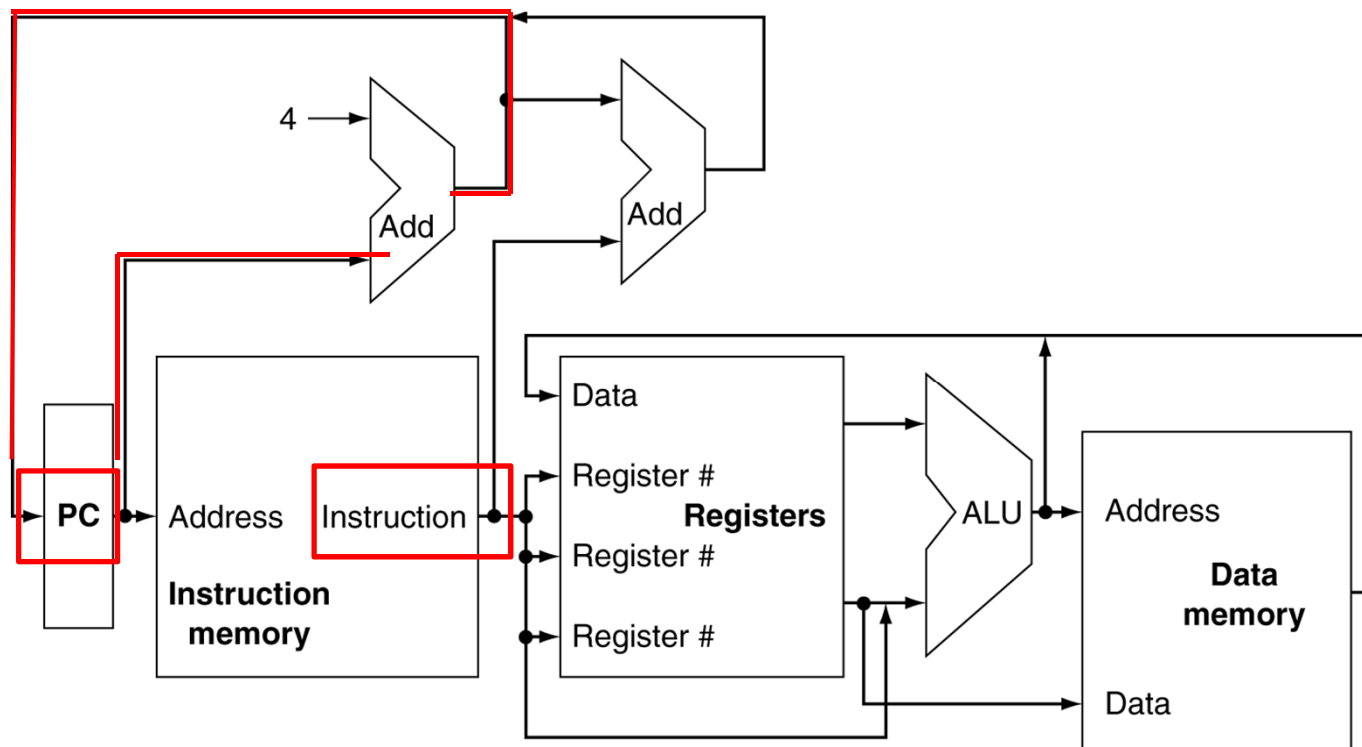- PC (Program counter) is used to fetch instruction in the **instruction** memory)
- After **instruction** is obtained, **register numbers** in instructions is used to read registers in register files.
- $PC \leftarrow PC + 4$ for sequentially execution



Different instructions have different actions



- Use **ALU** to calculate
 - Arithmetic result
 - Memory address for load/store
 - Branch target address
- Access data memory for load/store
- $PC \leftarrow$ target address

add \$t0, \$s1, \$s2


lw \$s1, 20(\$s2)

bne \$t0, \$s5, Exit


j Loop

 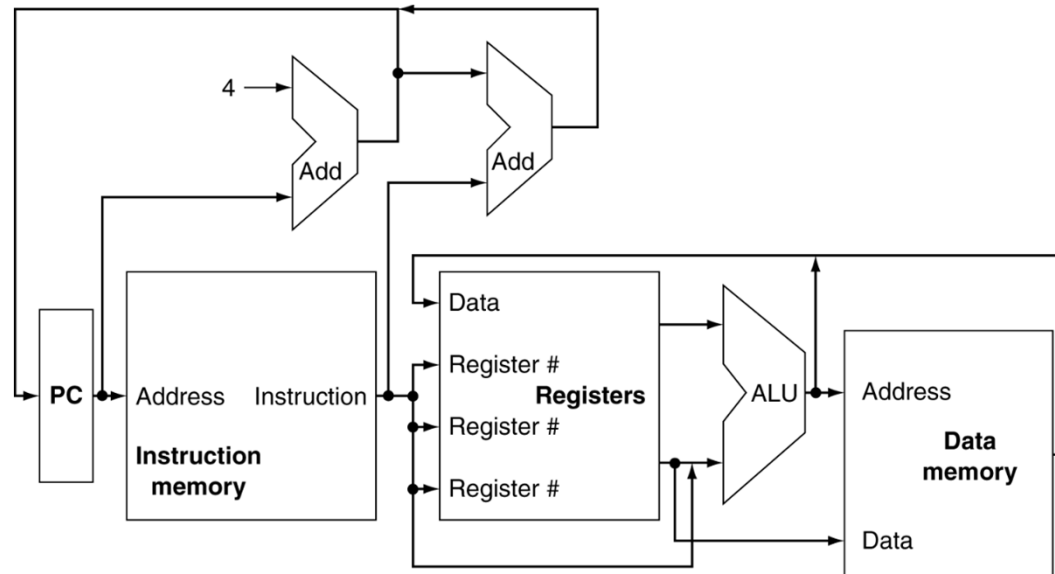


Need Multiplexers to fix problems

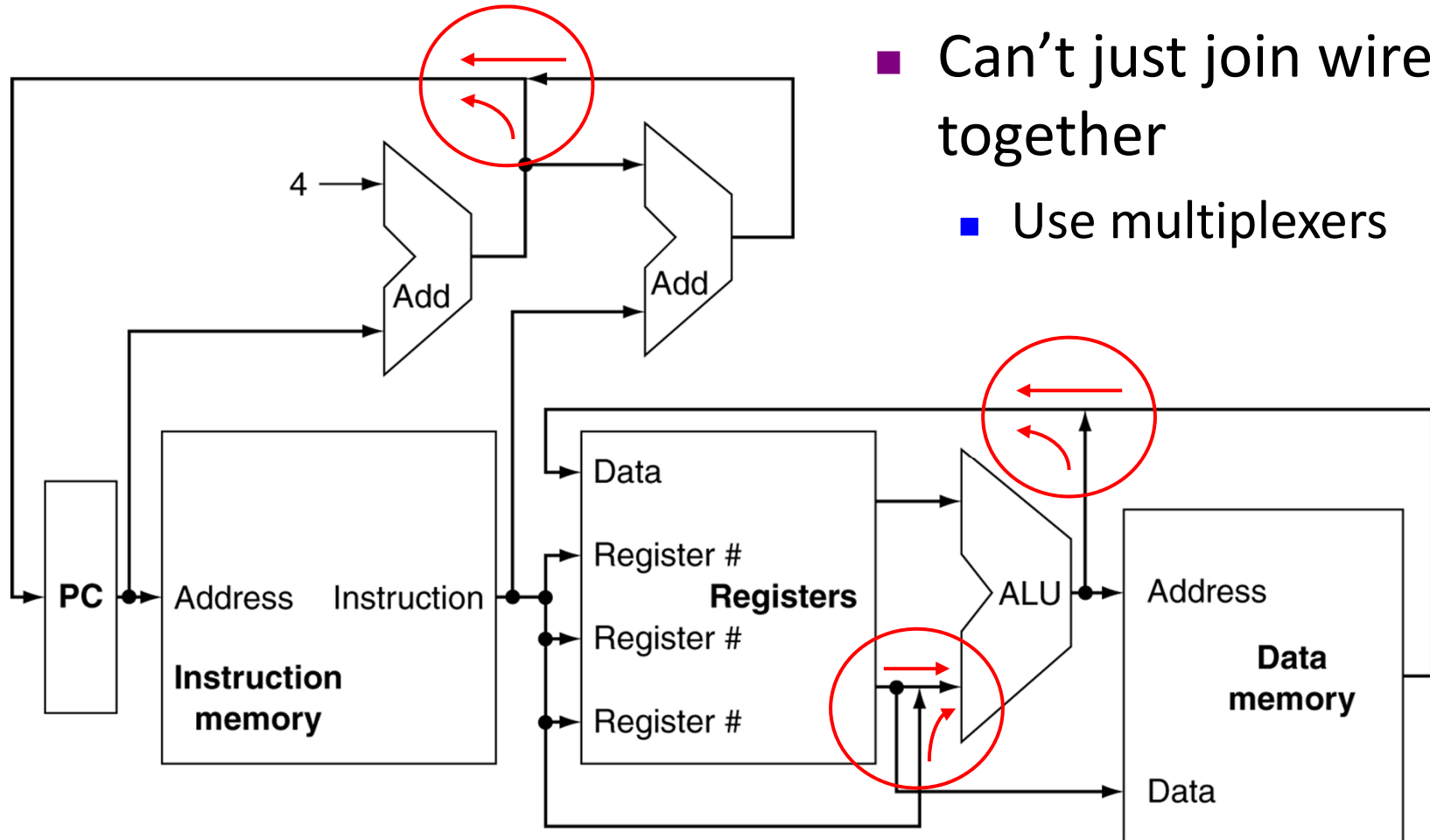

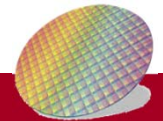- Can't just join wires together
 - Use multiplexers




Modified CPU– An overview

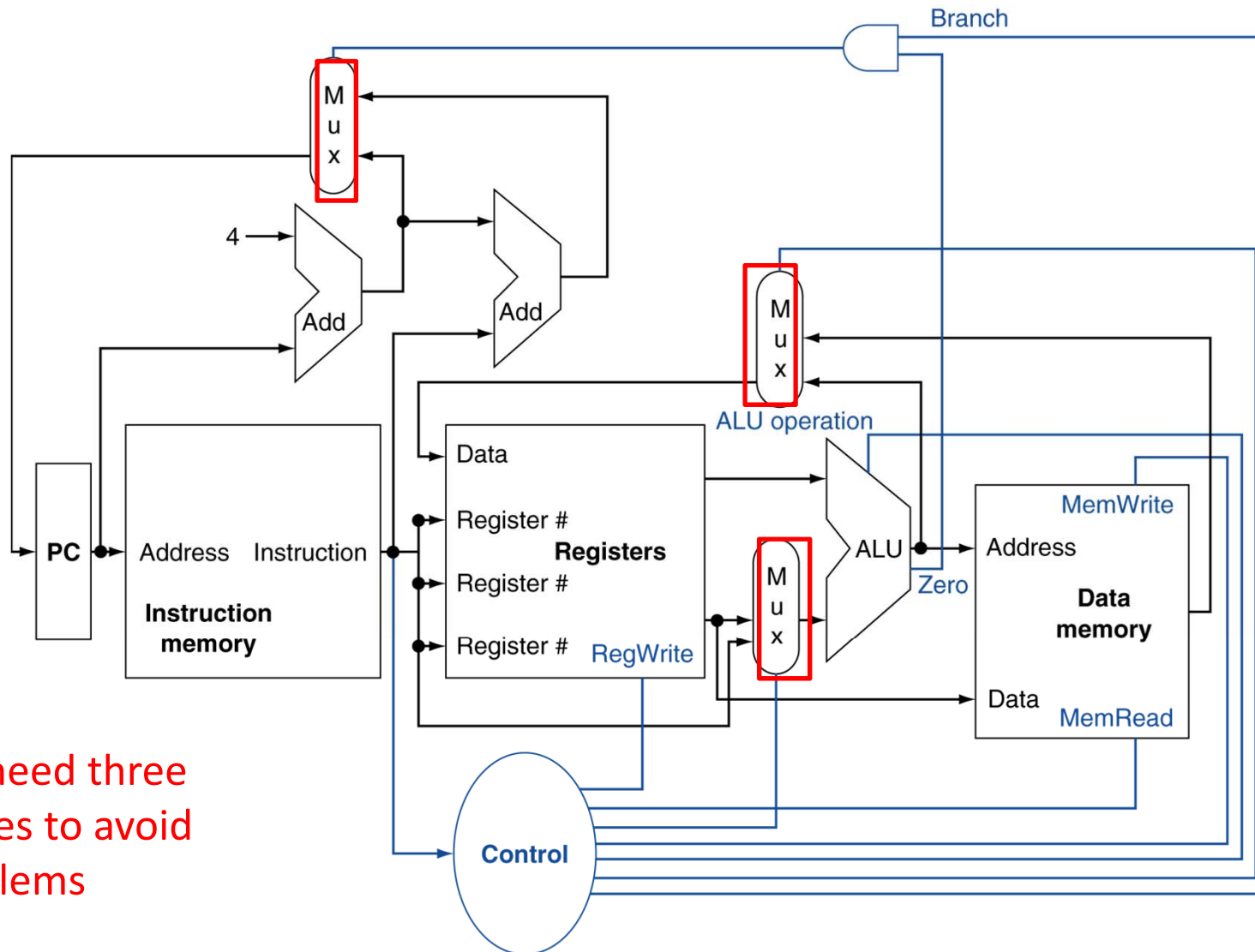


We need three
Muxes to avoid
problems

 
Details of each Mux and Control will be introduced later



Logic Design Basics

 
- Information encoded in binary
 - Low voltage = 0, High voltage = 1
 - One wire per bit
 - Multi-bit data encoded on multi-wire buses



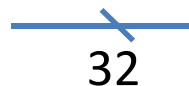 32-bit bus

A diagram showing a horizontal line representing a bus. A diagonal slash is drawn across the line, and the number 32 is written below the slash, indicating a 32-bit bus.

 
- Combinational element (See next slide)
 - Operate on data
 - Output is a function of input
- State (sequential) elements
 - Output is a function of input and current states
 - Store information



Review: Combinational Elements


- AND-gate

- $Y = A \& B$

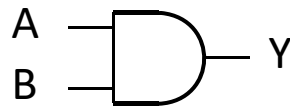


- Multiplexer

- $Y = S ? I1 : I0$

 



- Adder

- $Y = A + B$

 




- Arithmetic/Logic Unit

- $Y = F(A, B)$

  



Review: Sequential Elements

   - Register: stores data in a circuit
 - Uses a **clock** signal to determine when to update the stored value
 - **Edge-triggered**: update when **Clk** changes (0- \rightarrow 1 or 1- \rightarrow 0)
 - The following figure is **positive edge-triggered**: update when Clk changes from 0 to 1




Review: Sequential Elements (with write enable)

  - Register with write control
 - Only updates on clock edge when **write control** input is 1
 - Used when stored value is required later





Q is not changed when **Write=0**


 


Building a Datapath

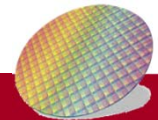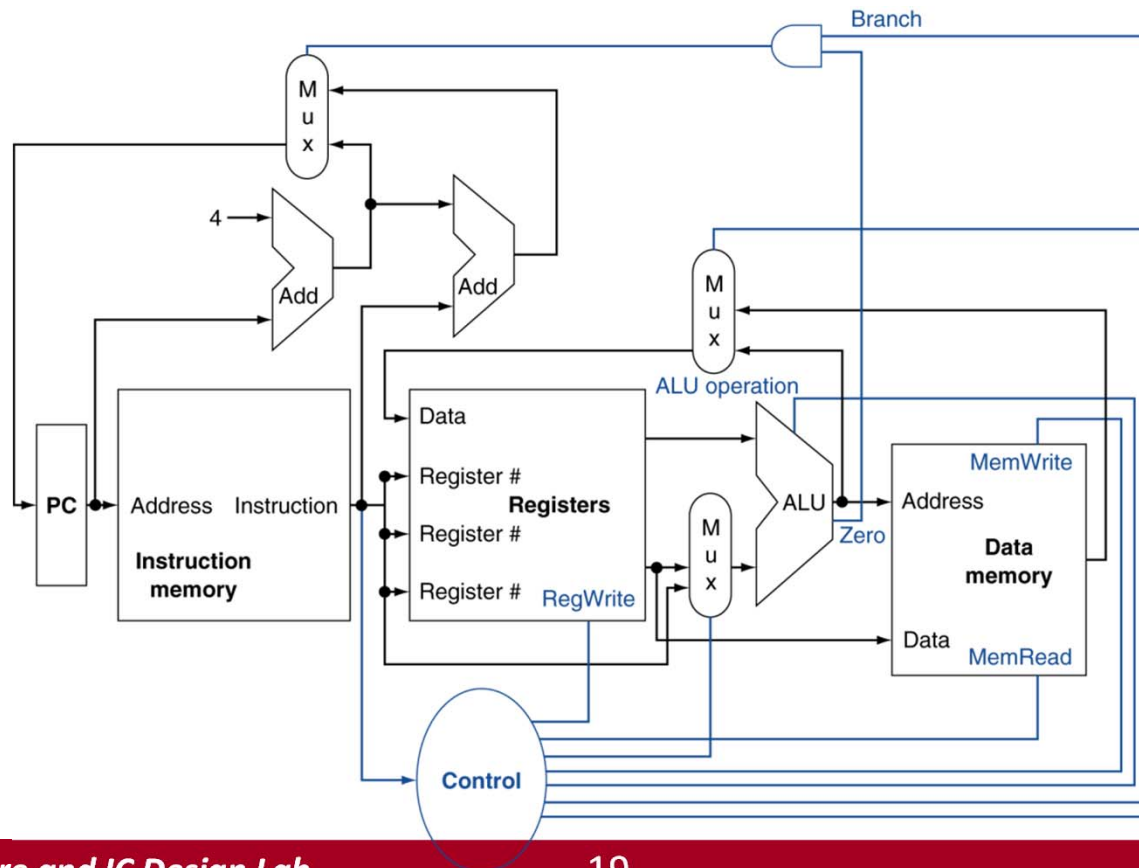- Datapath : Elements that process data and addresses in the CPU
 - Registers, ALUs, mux's, memories, ...
- We will show how to build MIPS datapath







Instruction Fetch

 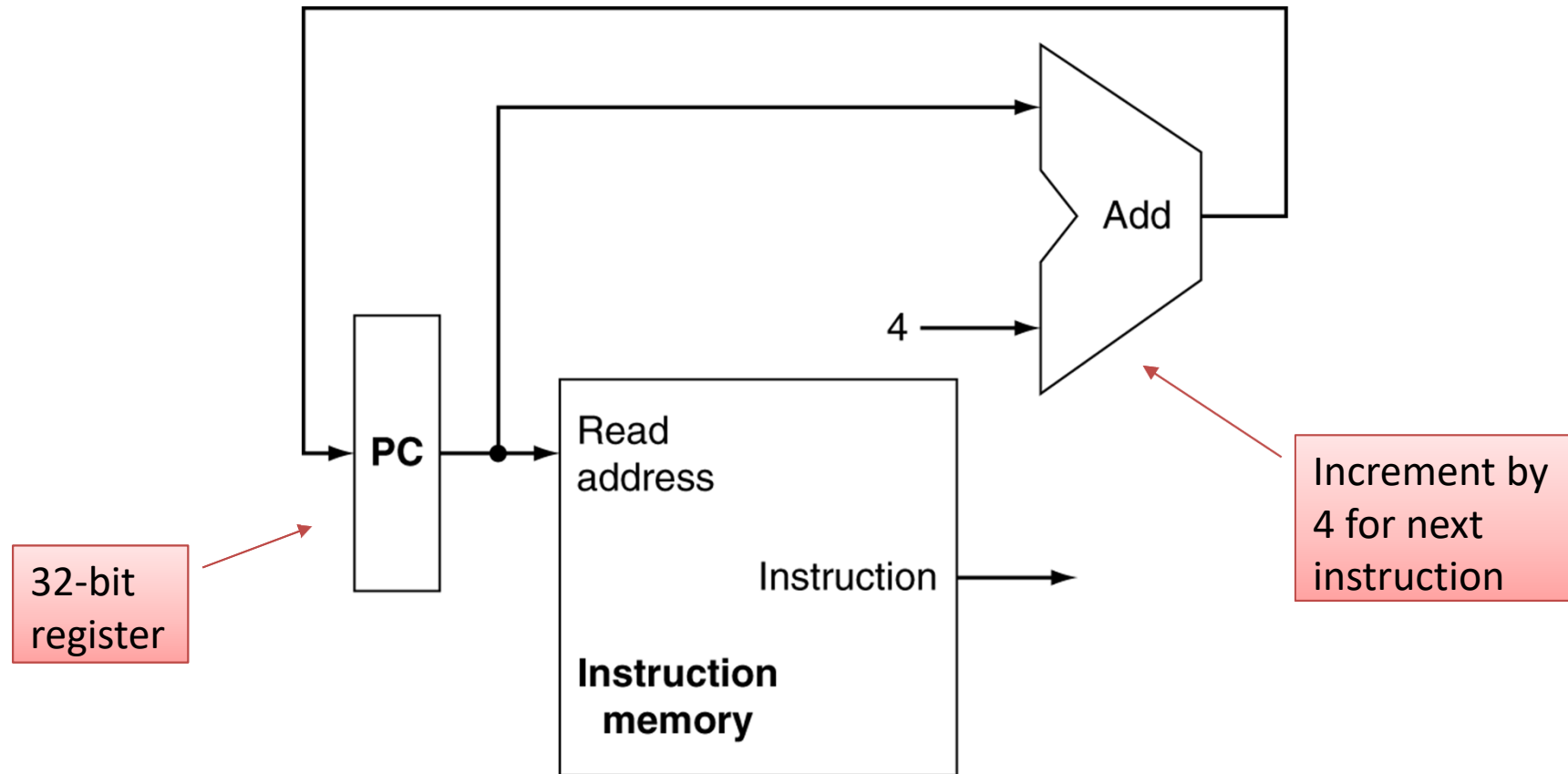

R-Format Instructions

 
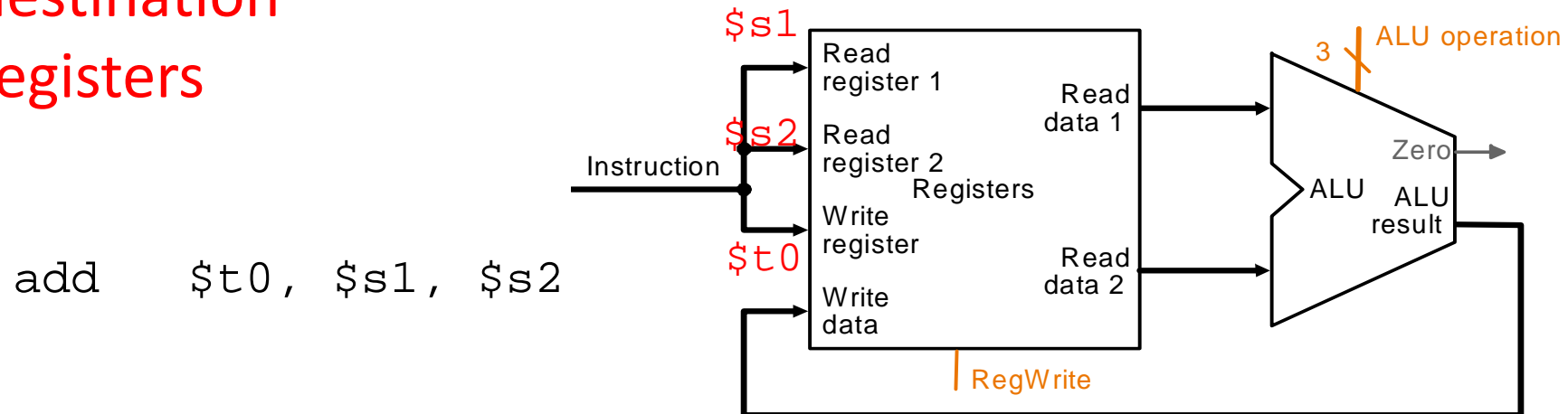
 
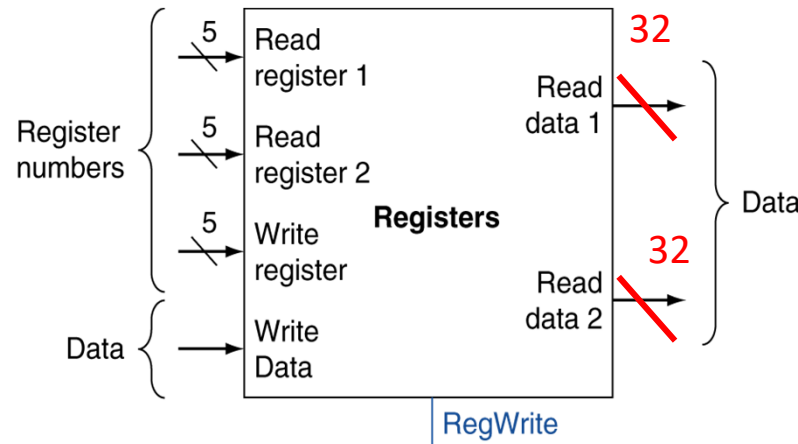
- Read two register operands
- Perform arithmetic/logical operation
- Write results into destination registers



Load/Store Instructions (need 4 components)


- Read register operands => register files
- Calculate address using 16-bit offset
 - Use **ALU**, but **sign-extend offset**
- Load/store: **read** memory and update register, and **write** register value to memory
 - Need data memory

   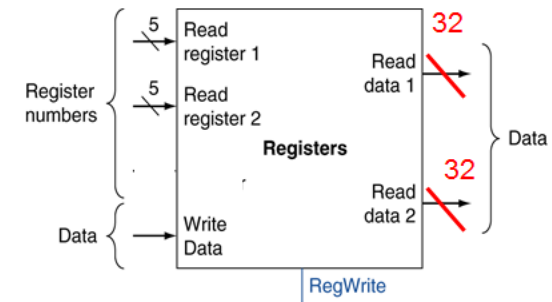lw \$t0, 4(\$s3) #load word from memory
sw \$t0, 8(\$s3) #store word to memory




Datapath: Load/Store Instruction

- Load/store

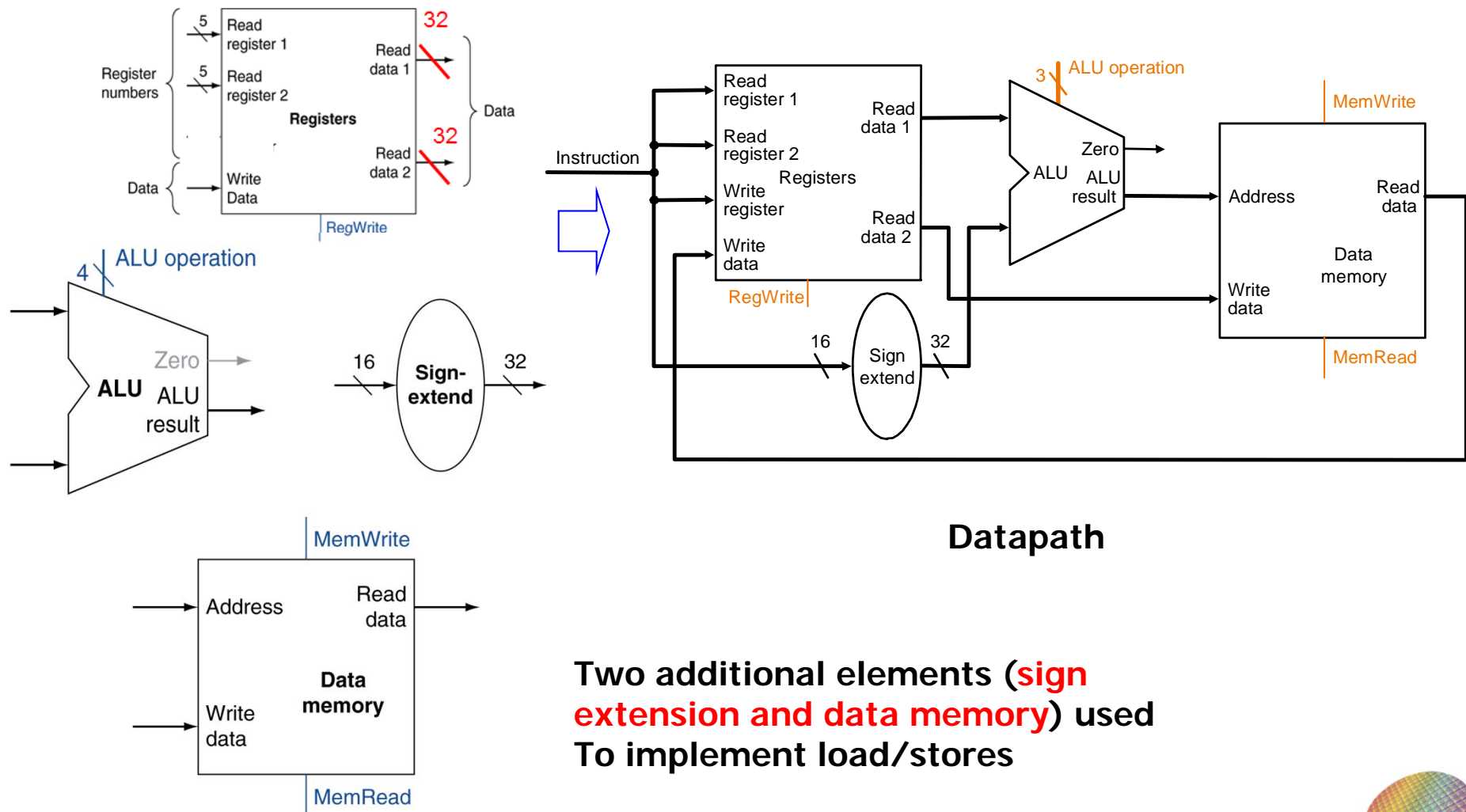

 Two additional elements (**sign extension** and **data memory**) used To implement load/stores



Animating the Datapath- load


- Load

e.g. `lw $t0, 4($s3)`

- RN1: register number 1
- RN2: register number 2
- WN: register number that will be written
- WD: write data

`lw rt, offset(rs)`

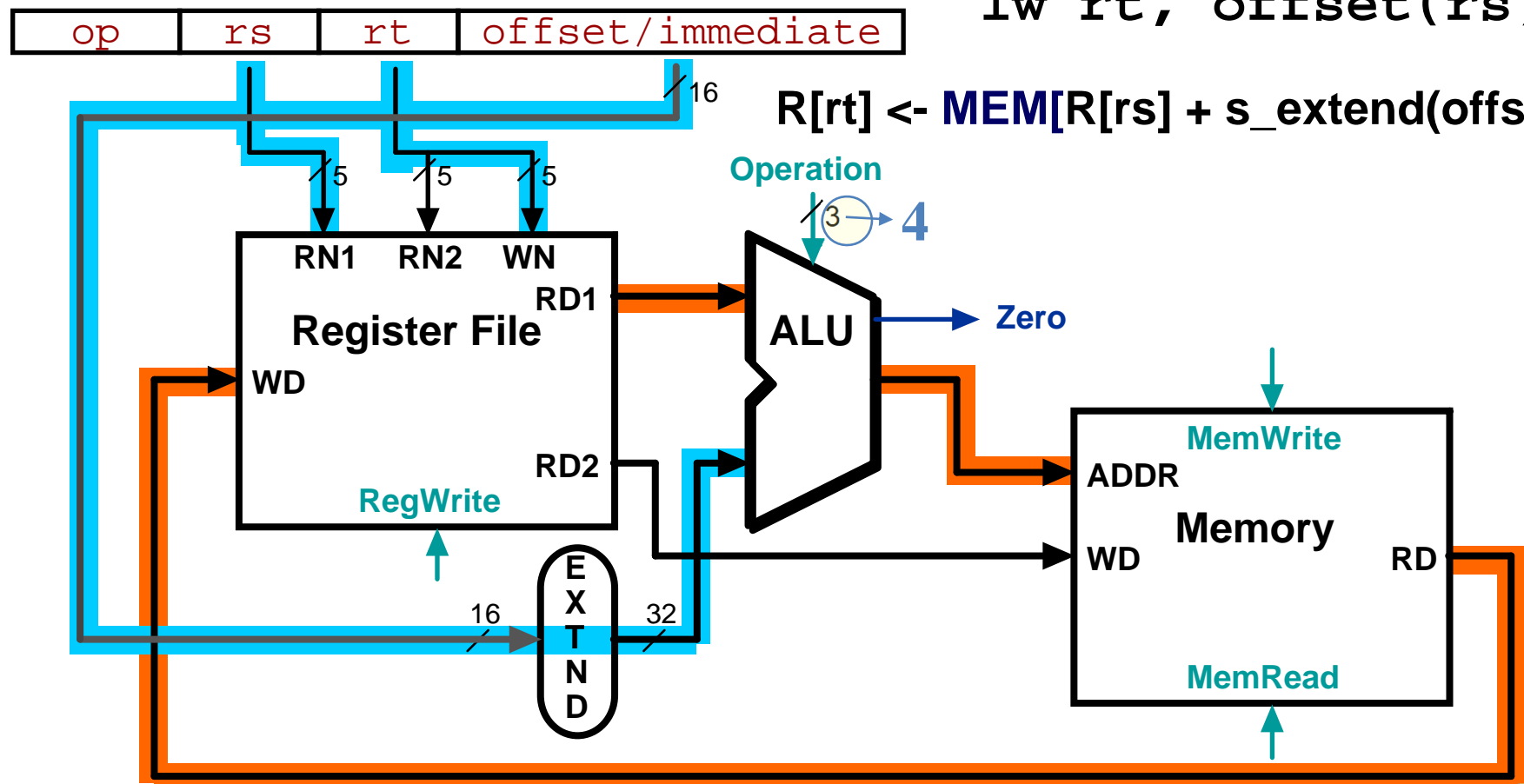$R[rt] \leftarrow \text{MEM}[R[rs] + \text{s_extend}(\text{offset})];$





Animating the Datapath- store

- store

`sw $t0, 8($s3)`

`sw rt, offset(rs)`

 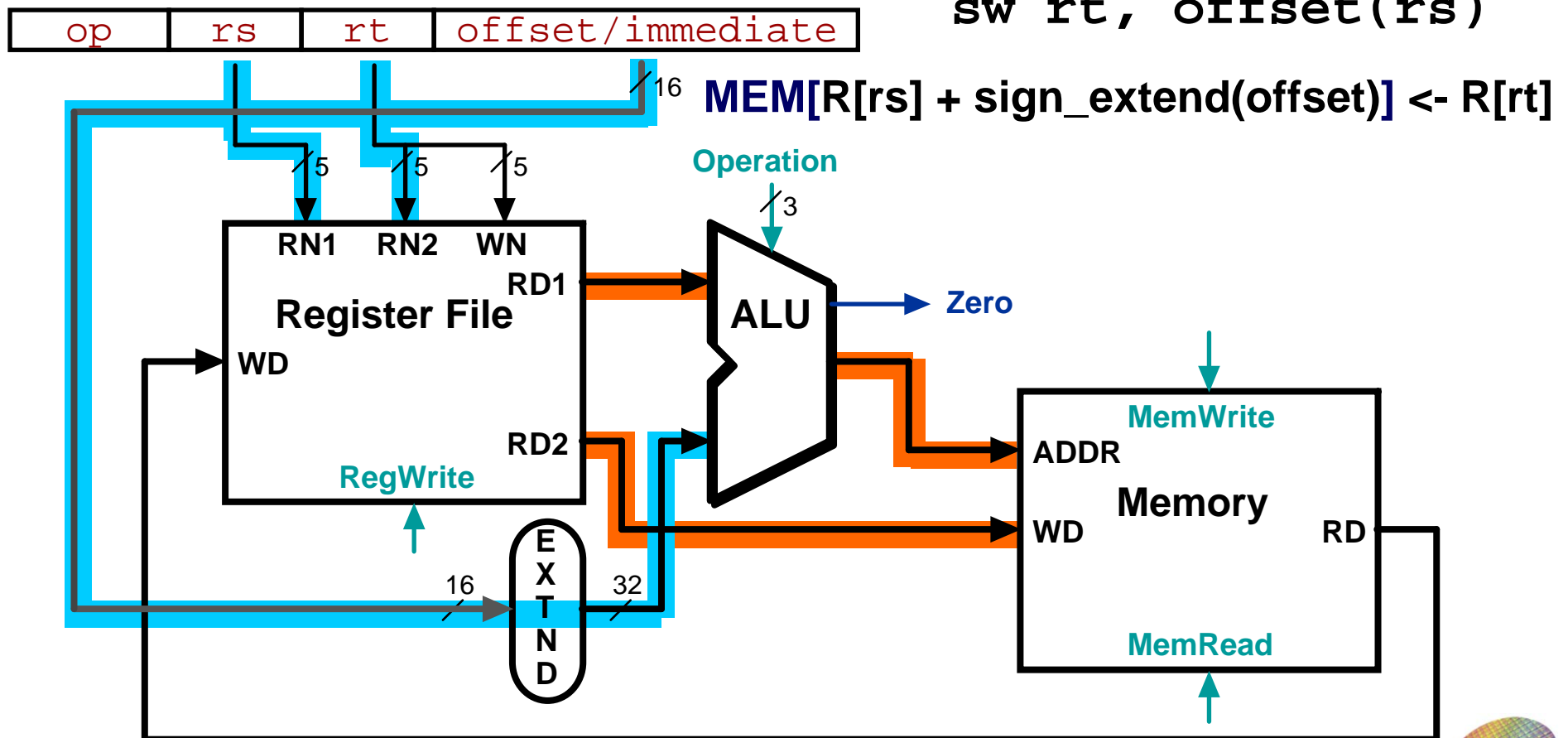

Review: Specifying Branch Destinations


- MIPS conditional branch instructions:



- PC-relative addressing

- Target address = $PC + \text{offset} \times 4$
- PC already incremented by 4 by this time

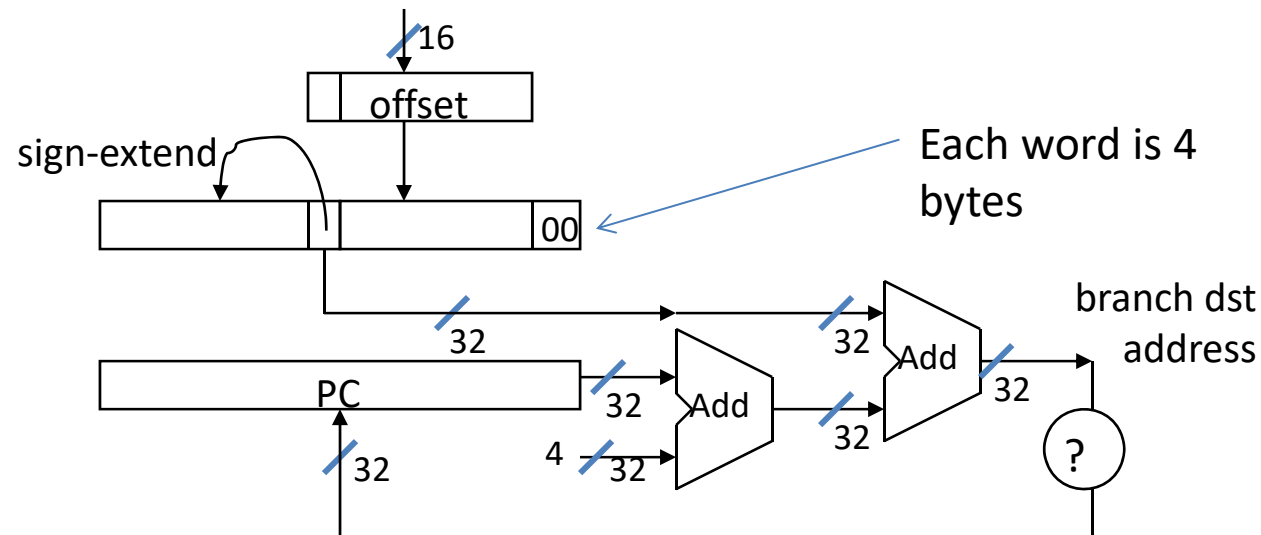from the low order 16 bits of the branch instruction



2000 beq \$s0 \$t1 2


2004

2008 ...

200C


Target Address (address of next instruction) =?

200C

 


Datapath: Branch Instructions

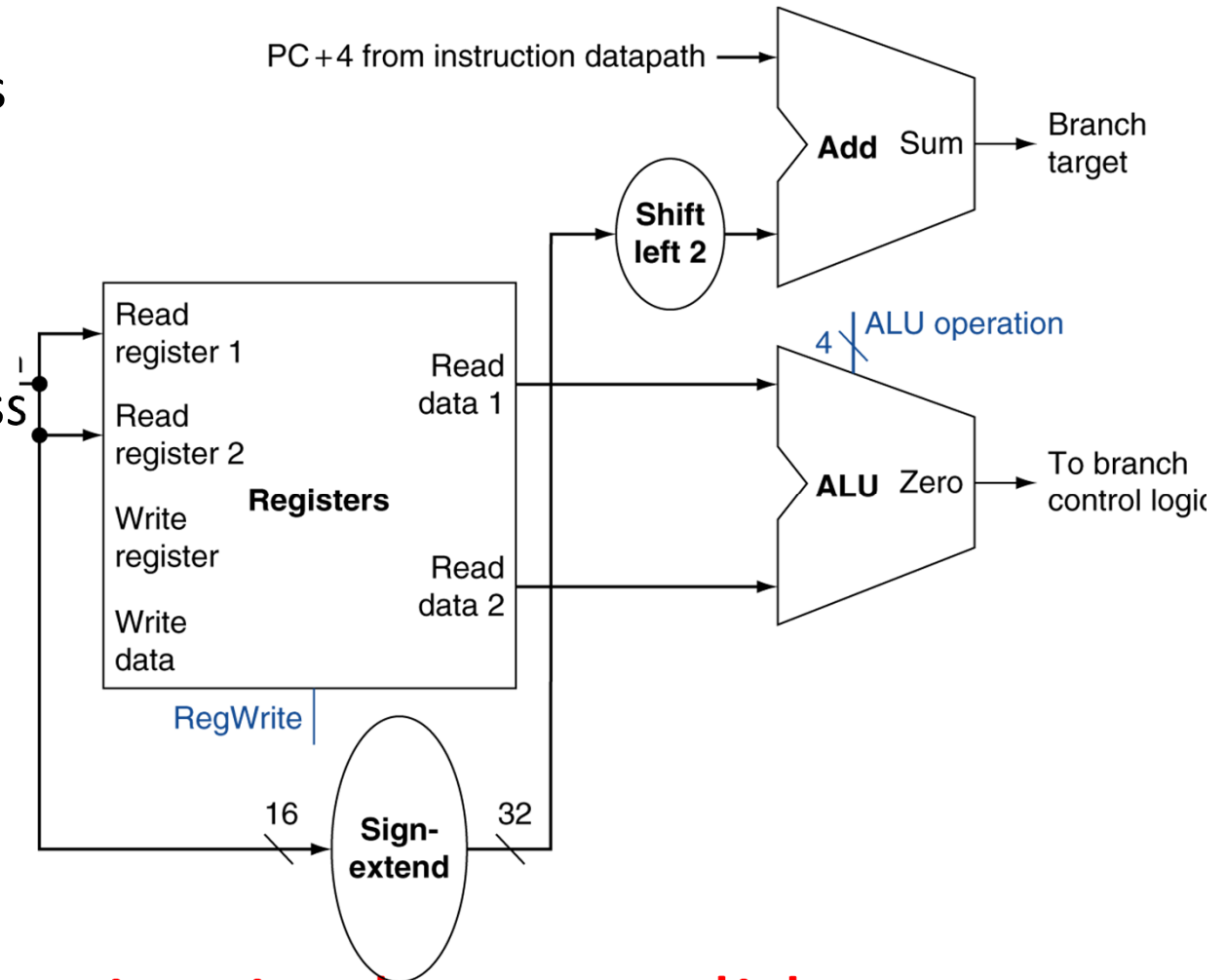- Read register operands
- Compare operands
 - Use **ALU**, subtract and check Zero output
- Calculate target address
 - **Sign-extend** offset
 - Shift left **2 bits** (word displacement)
 - Add to **PC + 4** (already calculated by instruction fetch)





See animation in the next slide

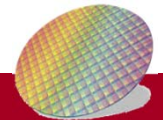

Animating the Datapath (beq)


- Beq rs, rt, offset

e.g. beq \$s0 \$t1 2

 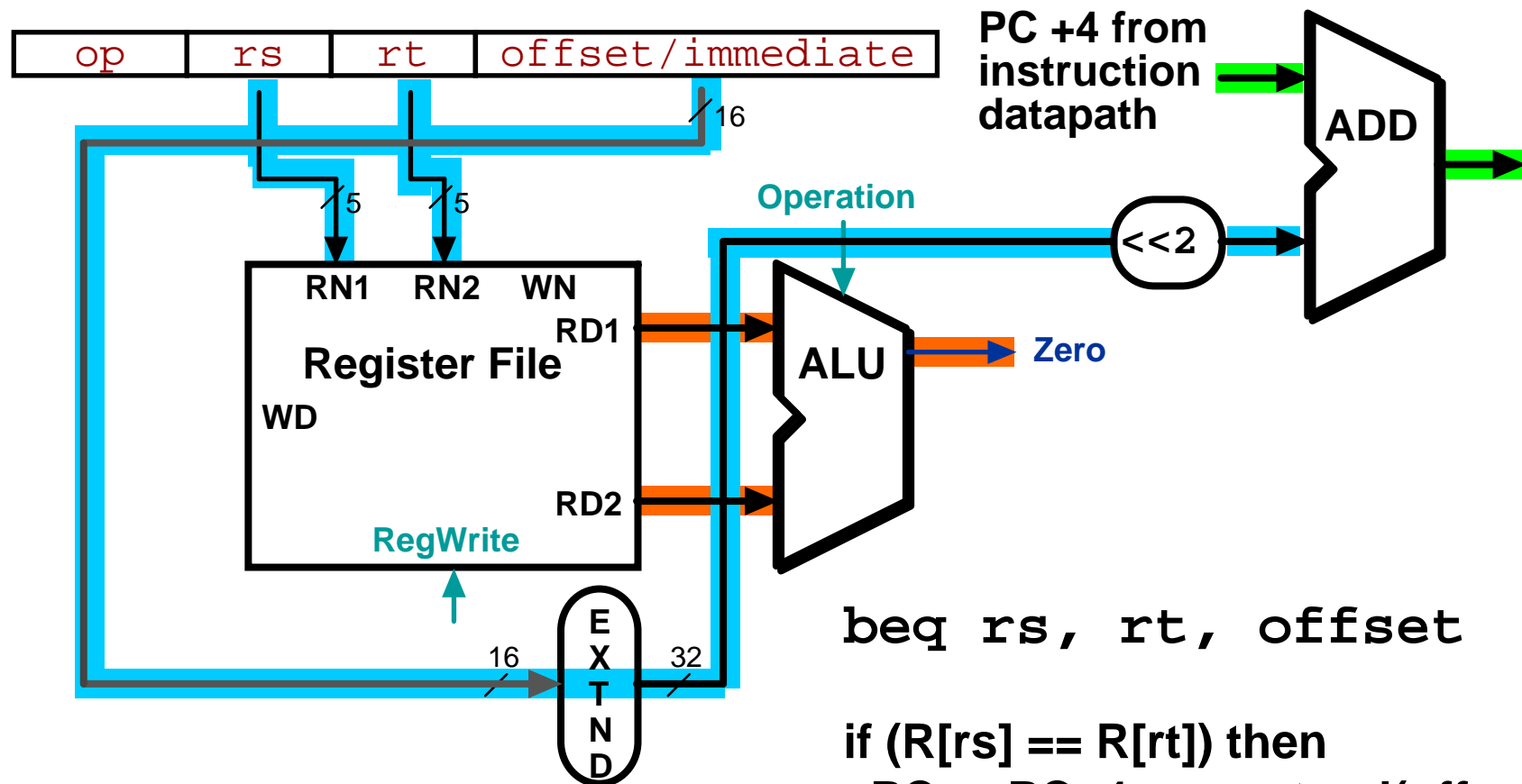


Sign-extension and shift left by 2 hardware

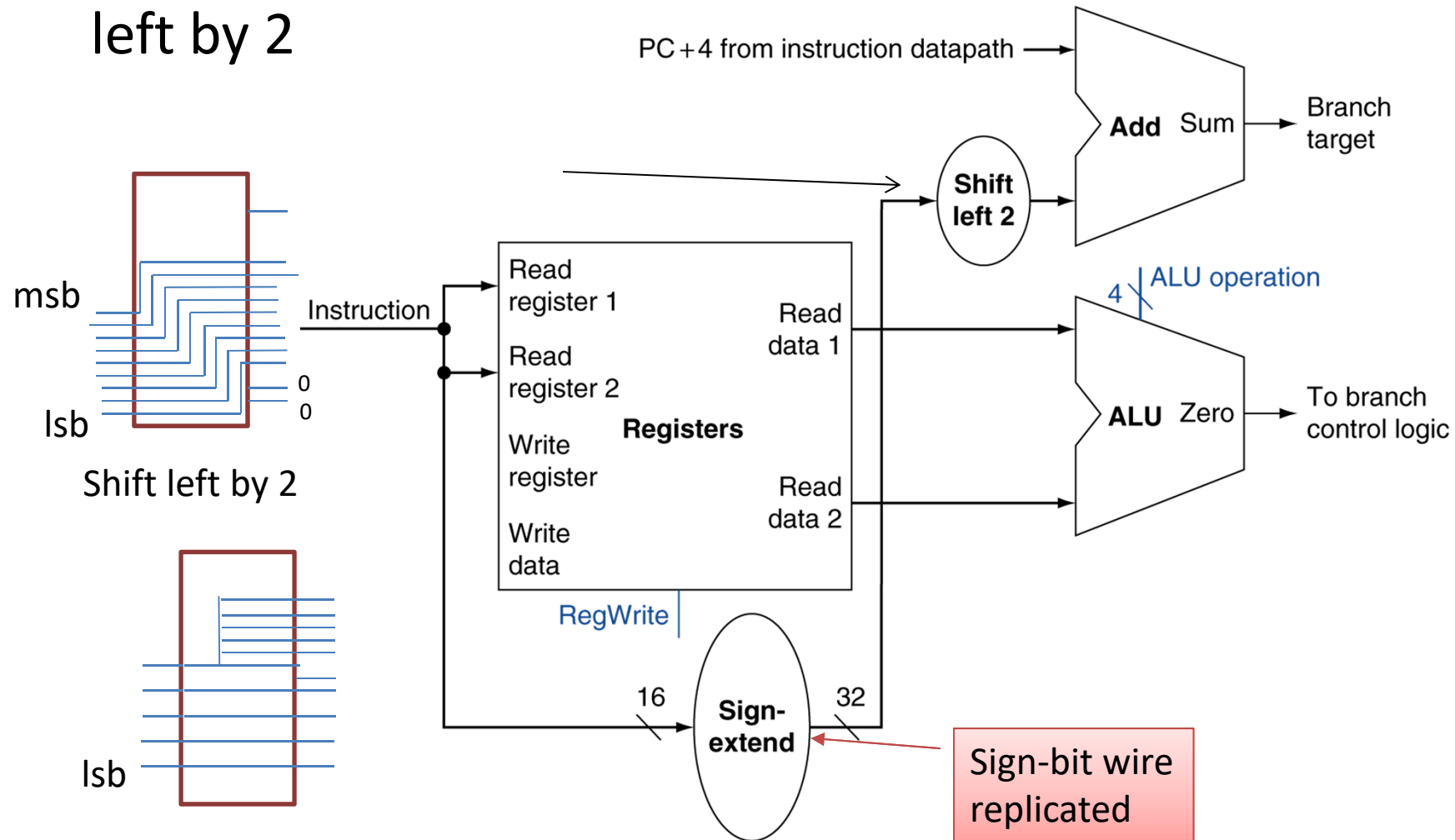- Simple hardware is used for sign extension and shift left by 2




Signed extension hardware

 


Composing the Elements

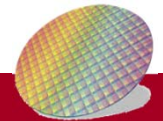- Make datapath do an instruction in **one clock cycle**
 - Each datapath **element** can only do **one** function at a time
 - Hence, we need **separate instruction** and **data** memories
- Use **multiplexers** where alternate data sources are used for different instructions




R-Type/Load/Store Datapath

A Single Cycle Datapath


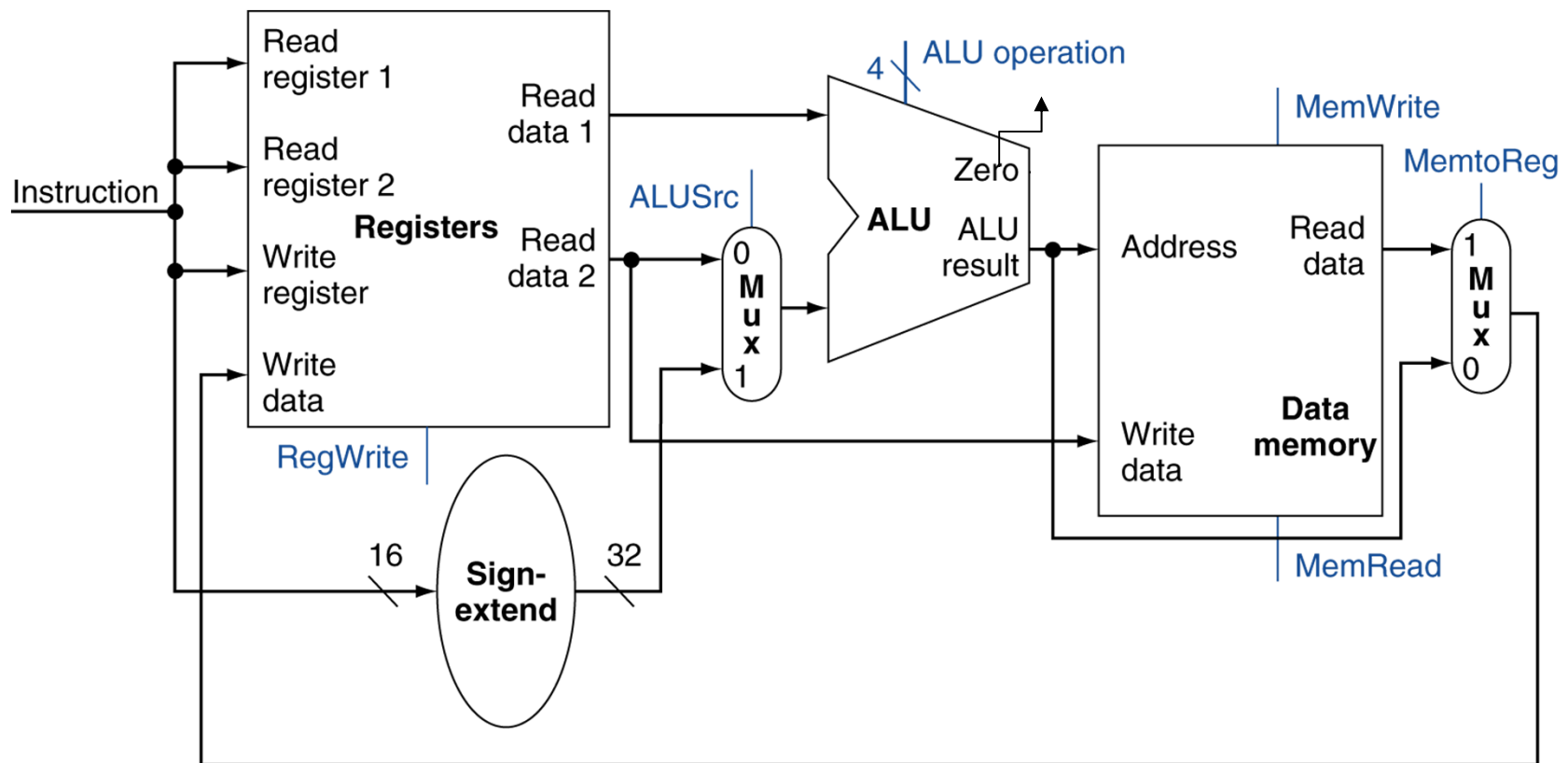


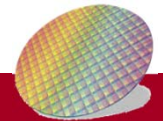Correct Control signal (RegWrite, ALUSrc, ALU operation, MemWrite, MemtoReg, MemRead) are needed to make sure correct operation is done






Full Datapath (Single Cycle Datapath)

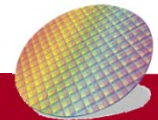
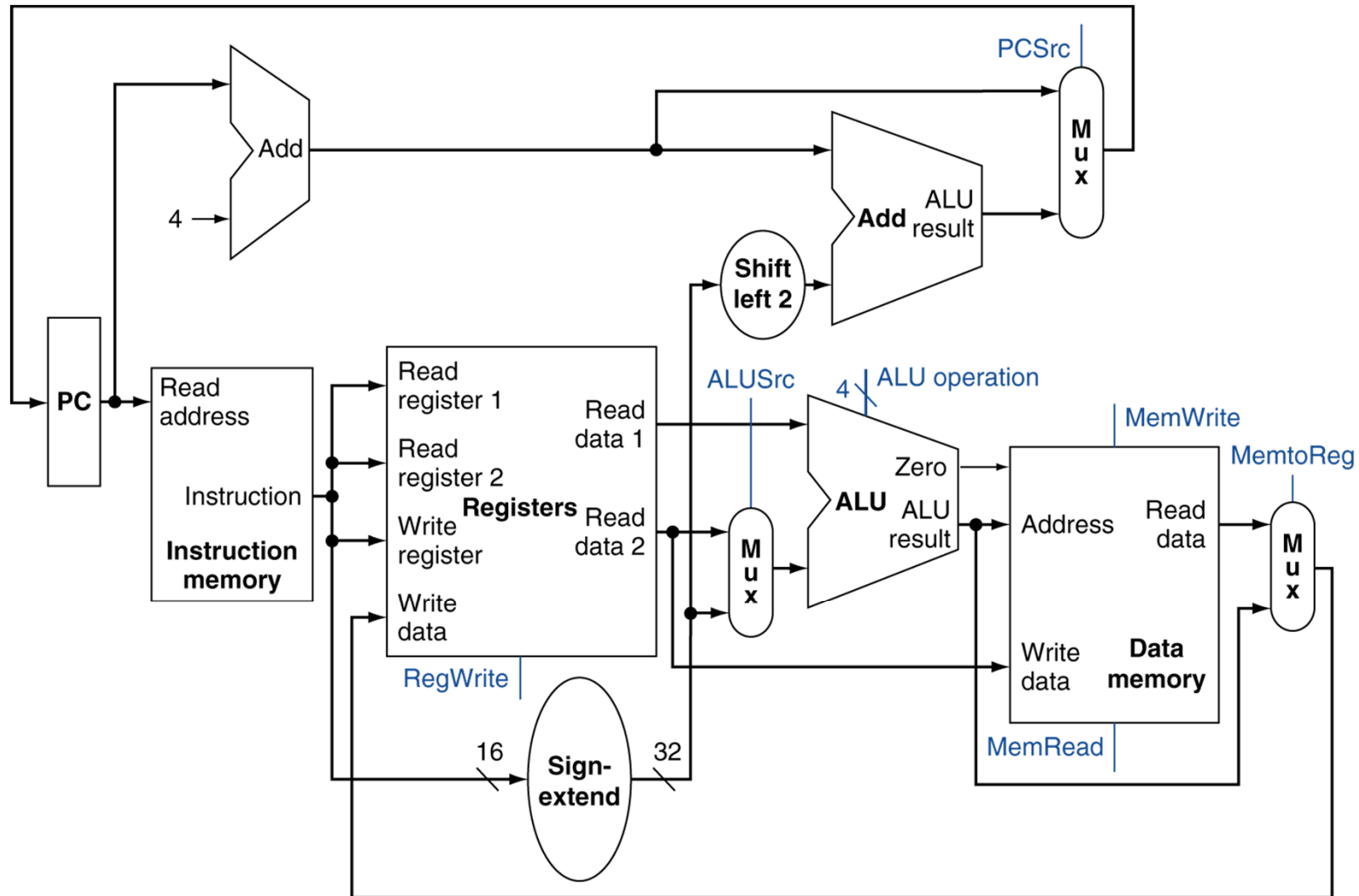


Control for the single-cycle CPU

 - A single-cycle implementation (the datapath)
 - R-type instruction (Arithmetic-logic instructions)
 - Memory instruction (load/store)
 - Branch
 - J-type instruction (j)
- Determine **control** for the single-cycle CPU to ensure instructions can be executed correctly
 - Main controller
 - ALU controller





Next: Building Datapath With Control

 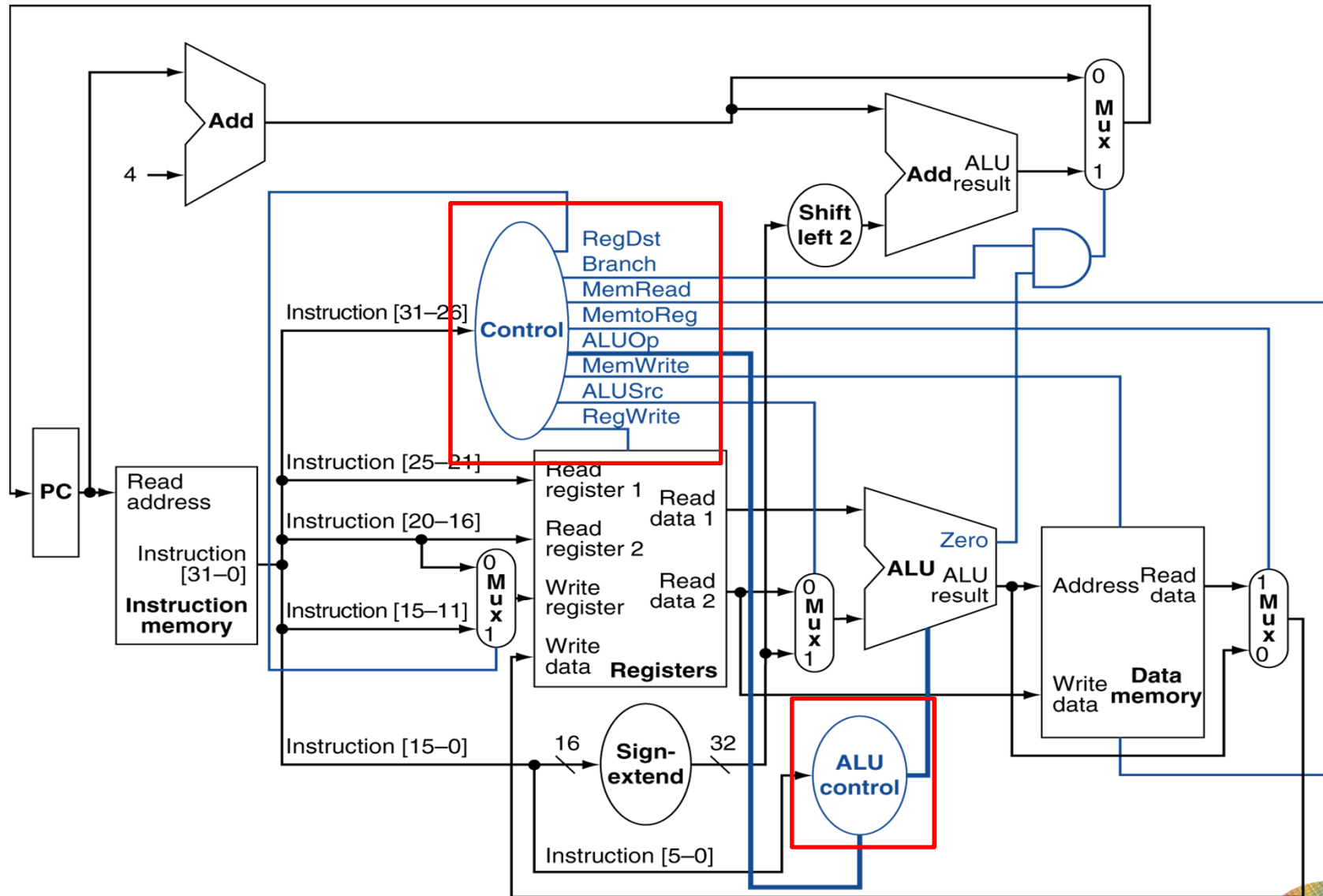



Main Control and ALU Control

 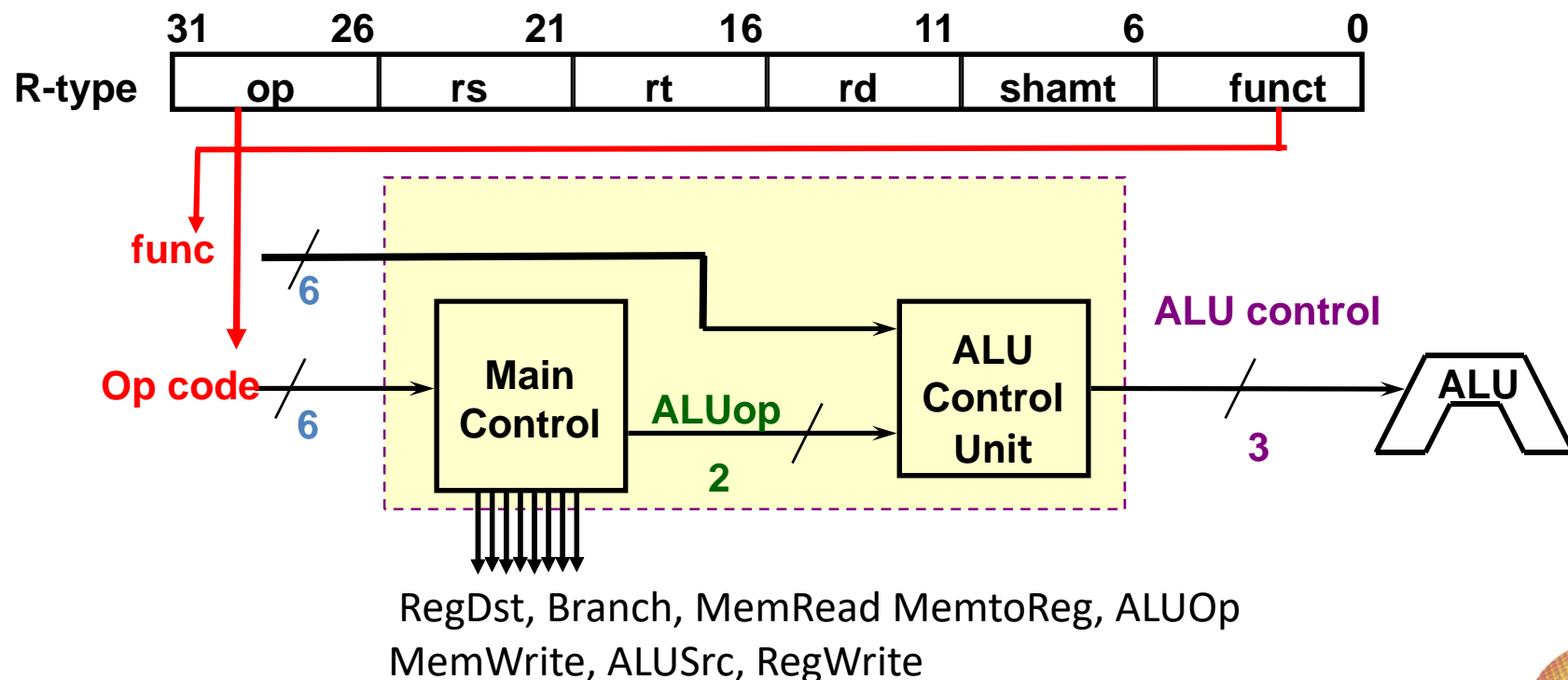
- **Main Control**: Based on opcode, generate RegDst, Branch, MemRead, MemtoReg, ALUOp, MemWrite, ALUSrc, RegWrite
- **ALU Control**: Based on 2-bit ALUOp and the 6-bit func field of instruction, the **ALU control unit** generates the 3-bit **ALU control** signal



Deciding ALU Control

- Assume 2-bit ALUOp derived from opcode
 - Combinational logic derives ALU control

opcode	Operation	funct	ALU function	ALU control
lw	load word	XXXXXX	add	?
sw	store word	XXXXXX	add	?
beq	branch equal	XXXXXX	subtract	?
R-type	add	100000	add	?
	subtract	100010	subtract	?
	AND	100100	AND	?
	OR	100101	OR	?
	set-on-less-than	101010	set-on-less-than	?


 


Review: 32-bit ALU in Chapter 3

- Binvert is compatible to CarryIn => Connect **Binvert** to CarryIn
=> is renamed to Bnegate
- Add **Zero detection circuit** => If all bit is 0 => Zero=1

Ainvert	Binvert	CarryIn	Op.	Func.
0	0	X	0	a and b
0	0	X	1	a or b
0	0	0	2	a + b
0	1	1	2	a - b
0	1	1	3	slt


Bnegate	Op[1:0]	Func.
0	00	a and b
0	01	a or b
0	10	a + b
1	10	a - b
1	11	slt

 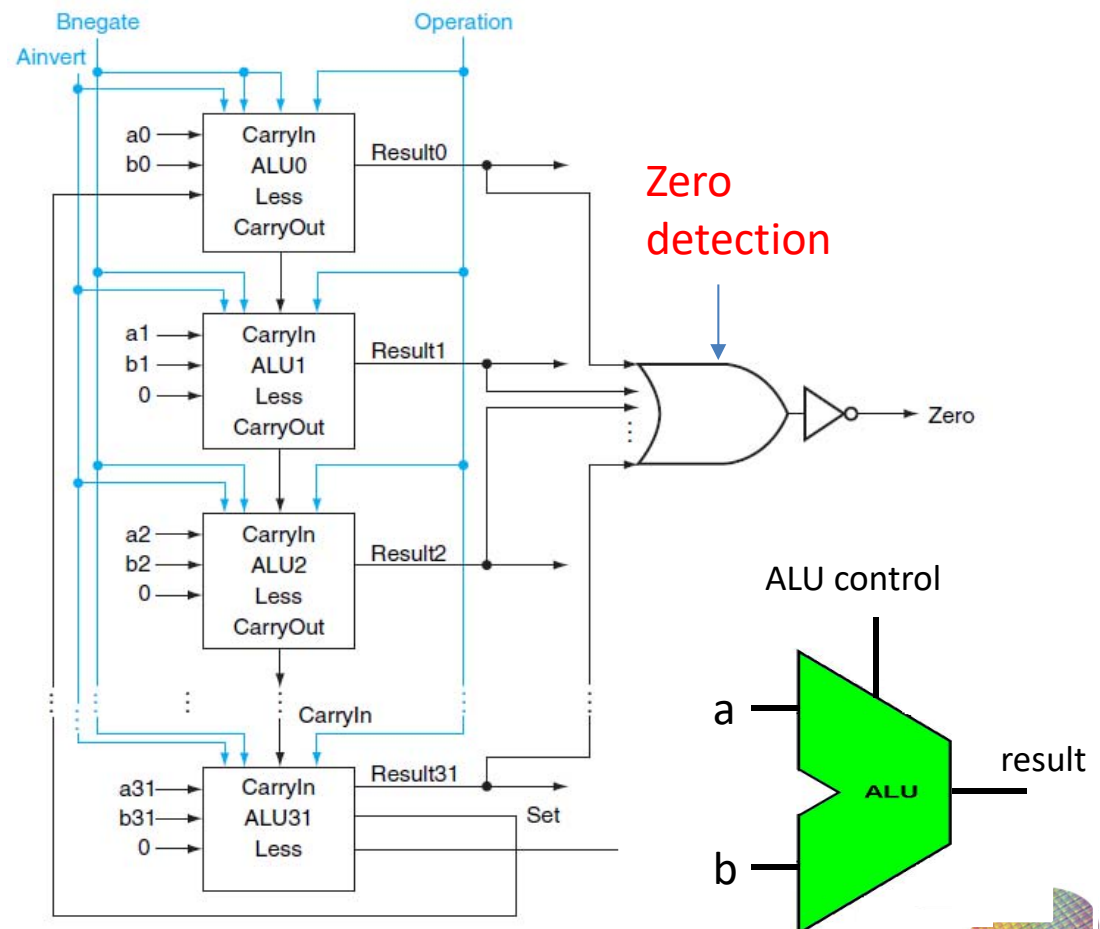

ALU Control



- ALU used for
 - Load/Store: function = add
 - Branch: function = subtract
 - R-type: function depends on **funct** field
- Assume **2-bit ALUOp** derived from opcode (generated by main controller)
 - Use ALUOp and funct to generate “ALU control” (discuss later)

opcode	ALUOp	Operation	funct	ALU function	ALU control
lw	00	load word	XXXXXX	add	010
sw	00	store word	XXXXXX	add	010
beq	01	branch equal	XXXXXX	subtract	110
R-type	10	add	100000	add	010
		subtract	100010	subtract	110
		AND	100100	AND	000
		OR	100101	OR	001
		set-on-less-than	101010	set-on-less-than	111

 



Determine Main Control Signals

- Control I signal

 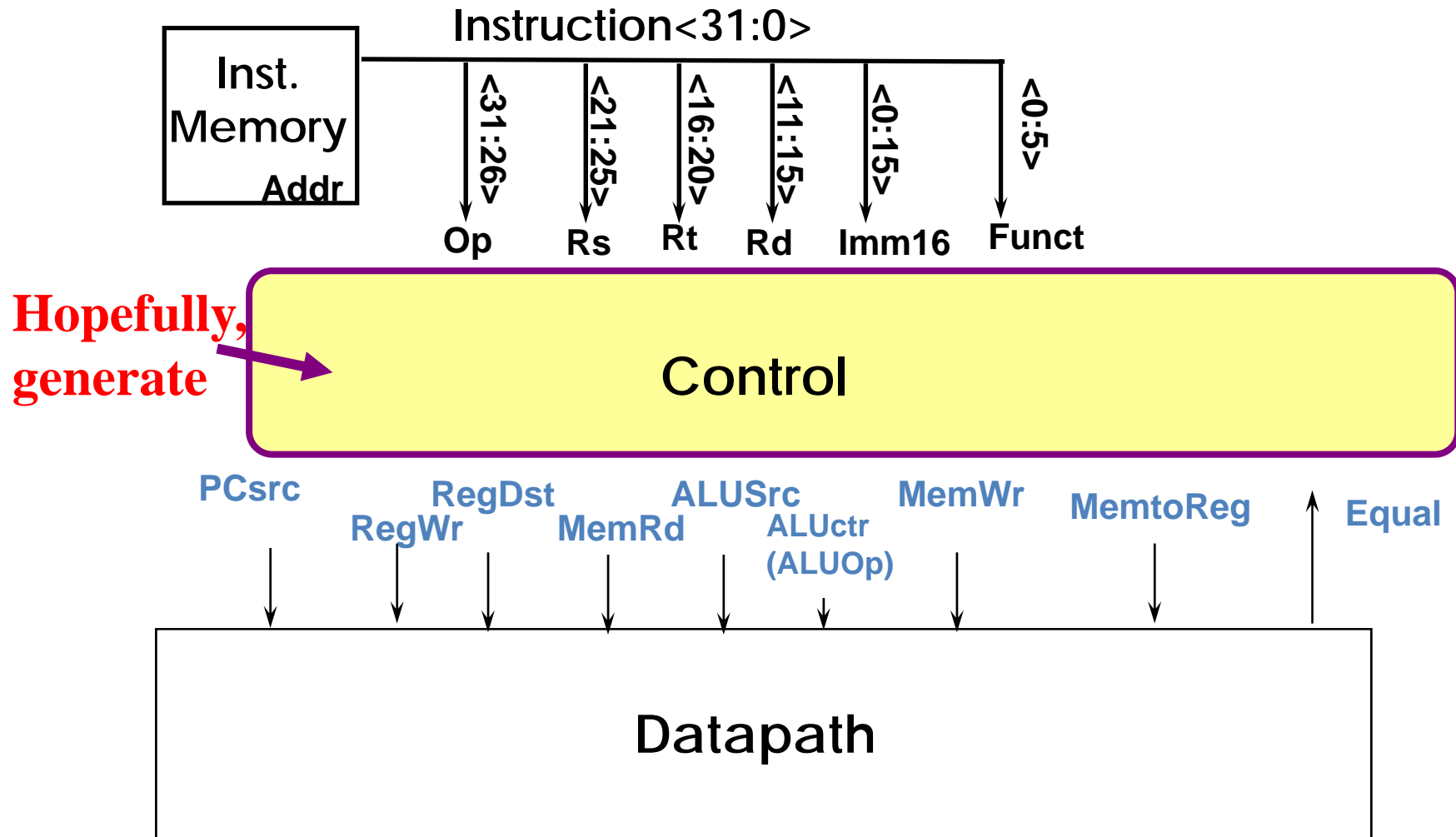


Review: The Main Control Unit

 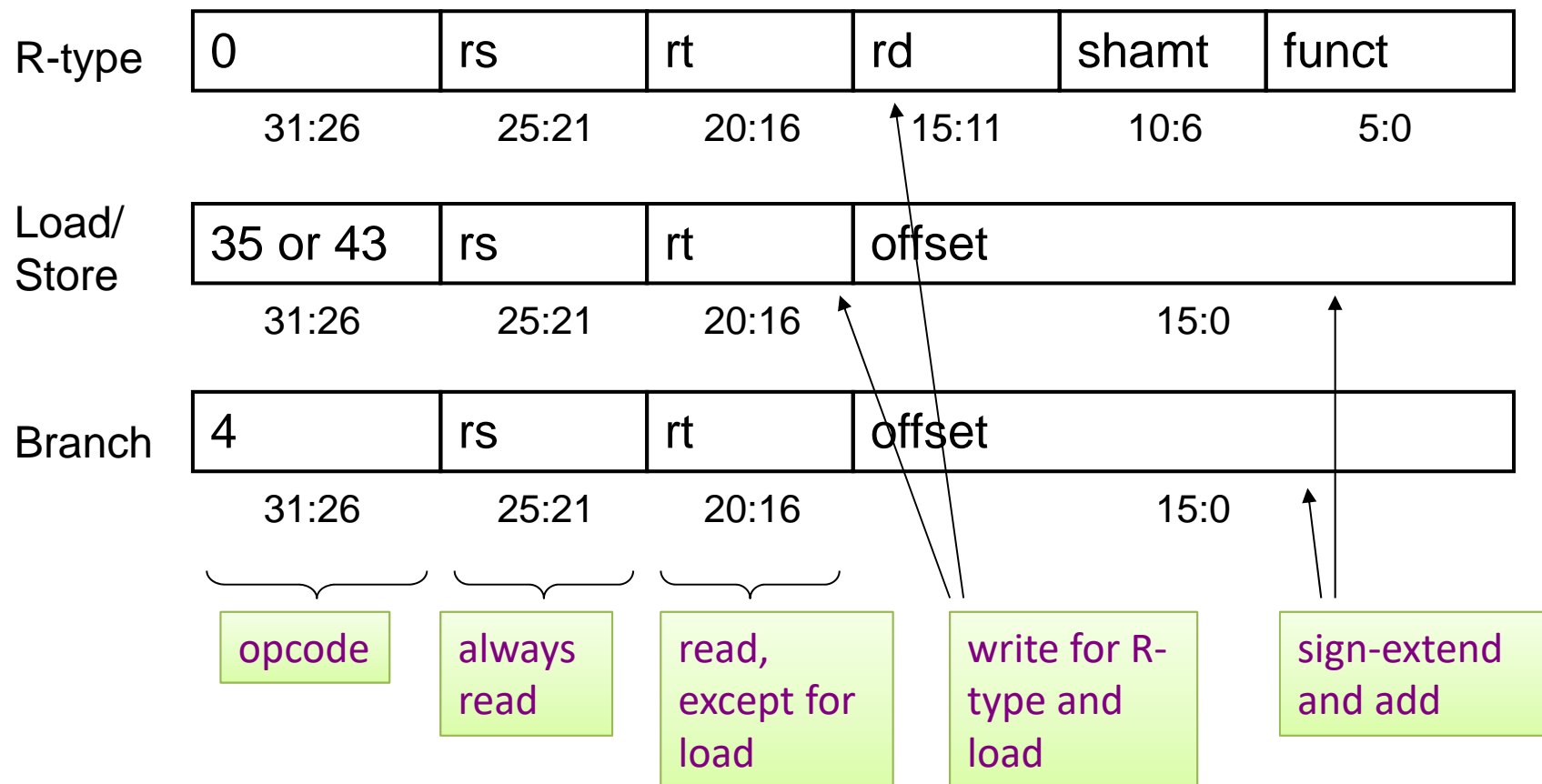
- Control signals derived from instruction





Control Signals for R-Type Instruction

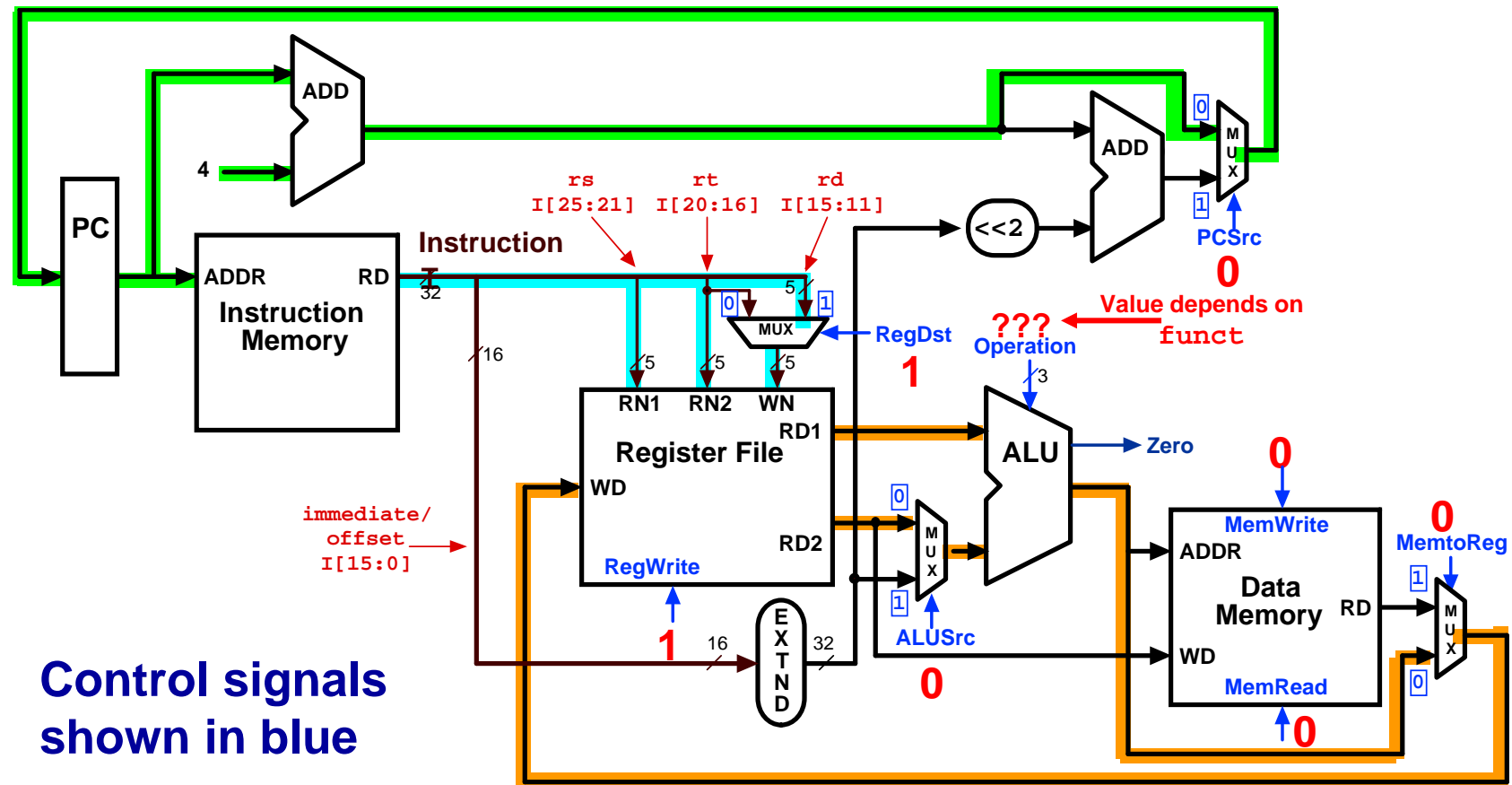


R-type	0	rs	rt	rd	shamt	funct
	31:26	25:21	20:16	15:11	10:6	5:0

 



Control Signals: lw Instruction

 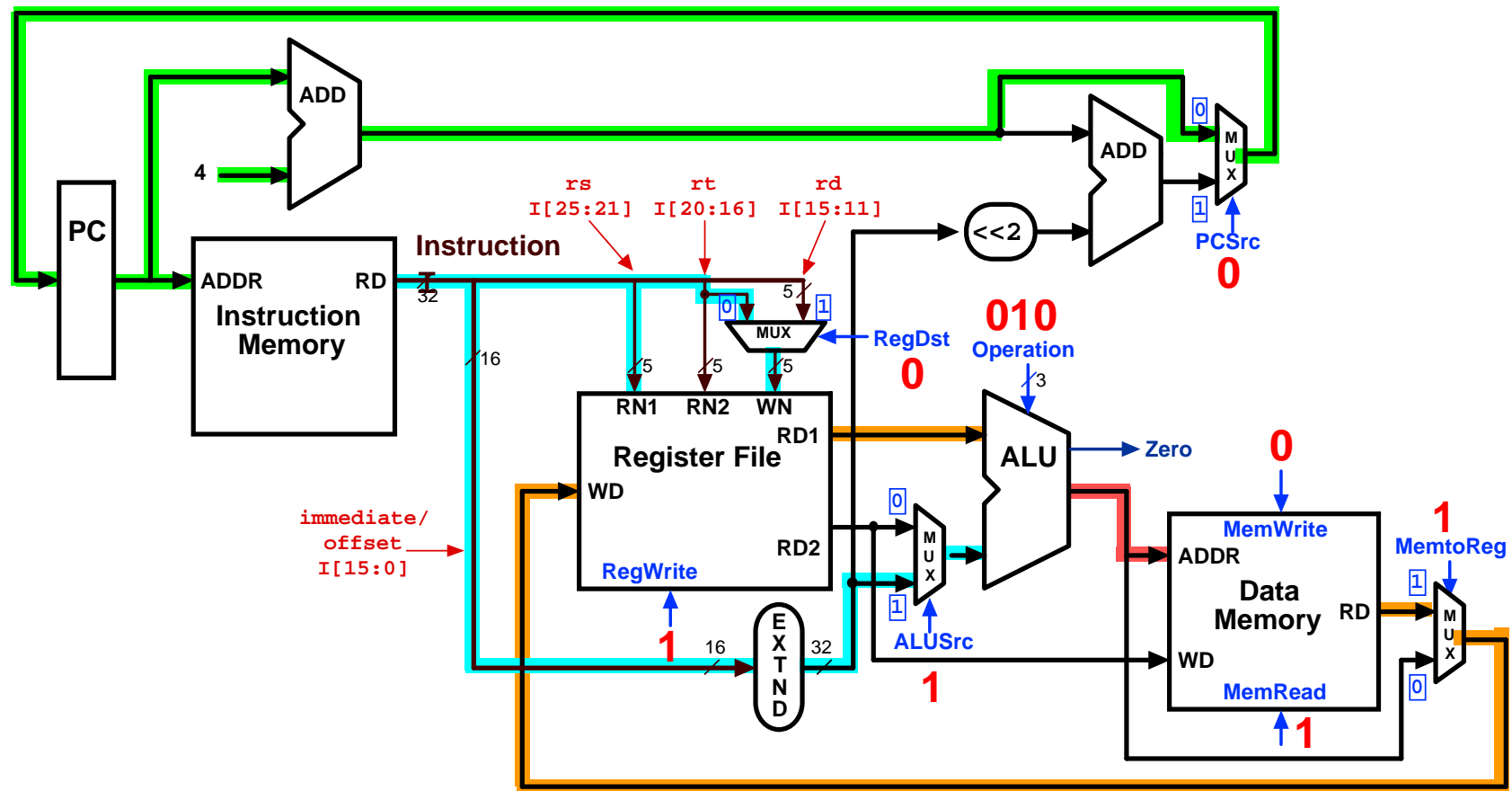


\$rt register is written

 




Control Signals: sw Instruction

 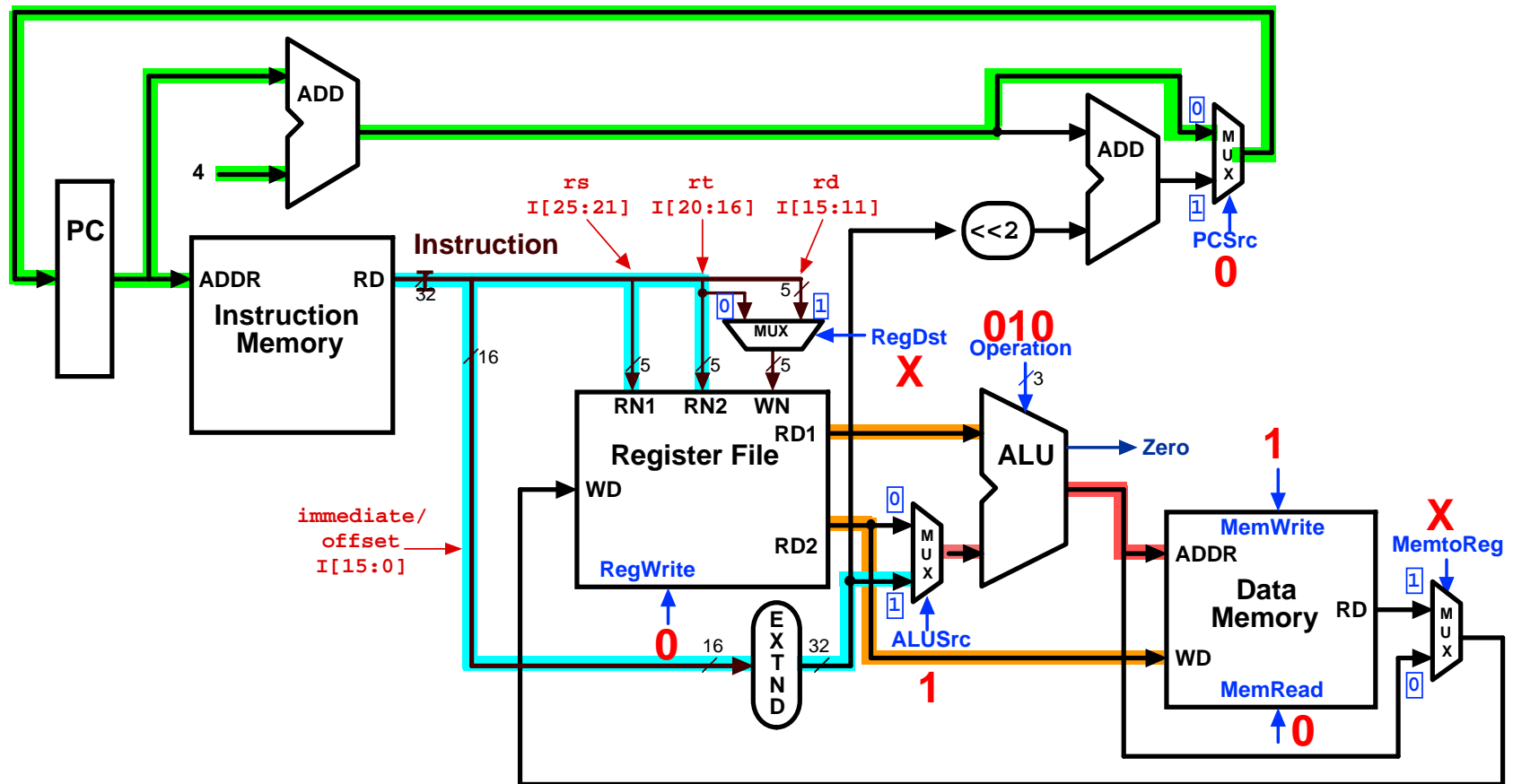


\$rt register is read

 



Control Signals: beq Instruction

  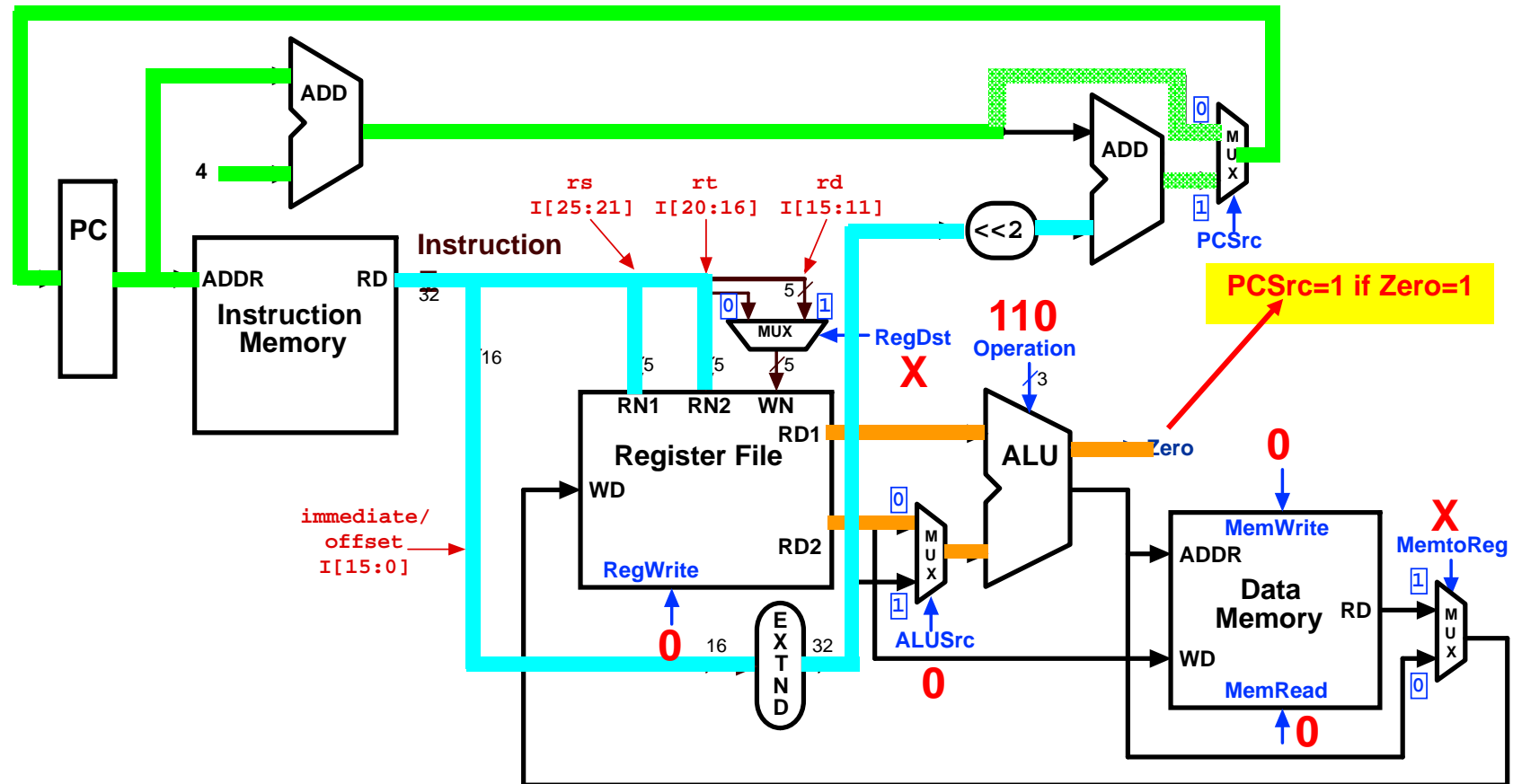

Review: Implementing Jumps

 


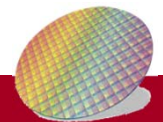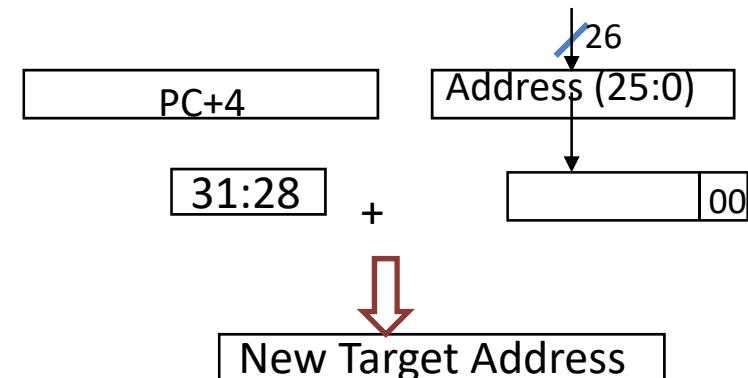- Jump uses **word** address
- Update **PC** with concatenation of
 - Top **4** bits of **old PC**
 - **26**-bit jump address
 - **00**
- Need an extra control signal decoded from opcode



Datapath Executing j instruction

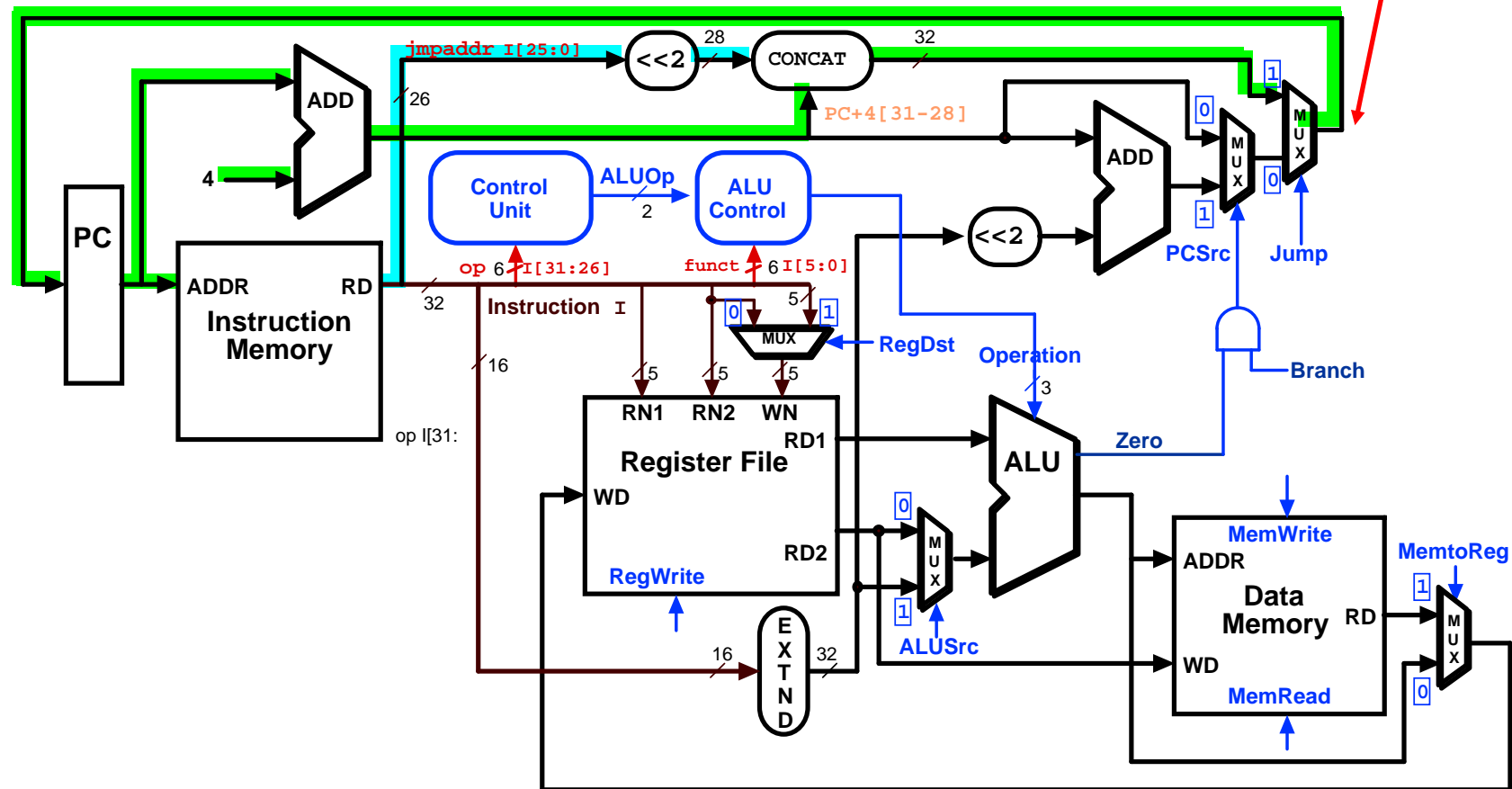Mux for Jump Inst
Jump=1 if it is a jump instruction




Jump

2

address

31:26

25:0

 


Truth Table for Main Control Signals

- Current design of control is for
 - lw, sw, beq, and, or, add, sub, slt
- I-format: lw, sw, beq
- R-format: and, or, add, sub, slt
- Given 4 OP codes (each has 6 bits) as “inputs”, the “outputs” are as follows => a main control logic (the next slide)


See **appendix D**
for details

inputs			outputs						
Instruction	RegDst	ALUSrc	Memto-Reg	Reg Write	Mem Read	Mem Write	Branch	ALUOp1	ALUOp0
R-format 000000	1	0	0	1	0	0	0	1	0
lw 100011	0	1	1	1	1	0	0	0	0
sw 101011	X	1	X	0	0	1	0	0	0
beq 000100	X	0	X	0	0	0	1	0	1

 

Implementation of Main Control Block (Use PLA)

	Signal name	R-format	lw	sw	beq
Inputs	Op5	0	1	1	0
	Op4	0	0	0	0
	Op3	0	0	1	0
	Op2	0	0	0	1
	Op1	0	1	1	0
	Op0	0	1	1	0
Outputs	RegDst	1	0	x	x
	ALUSrc	0	1	1	0
	MemtoReg	0	1	x	x
	RegWrite	1	1	0	0
	MemRead	0	1	0	0
	MemWrite	0	0	1	0
	Branch	0	0	0	1
	ALUOp1	1	0	0	0
	ALUOp0	0	0	0	1

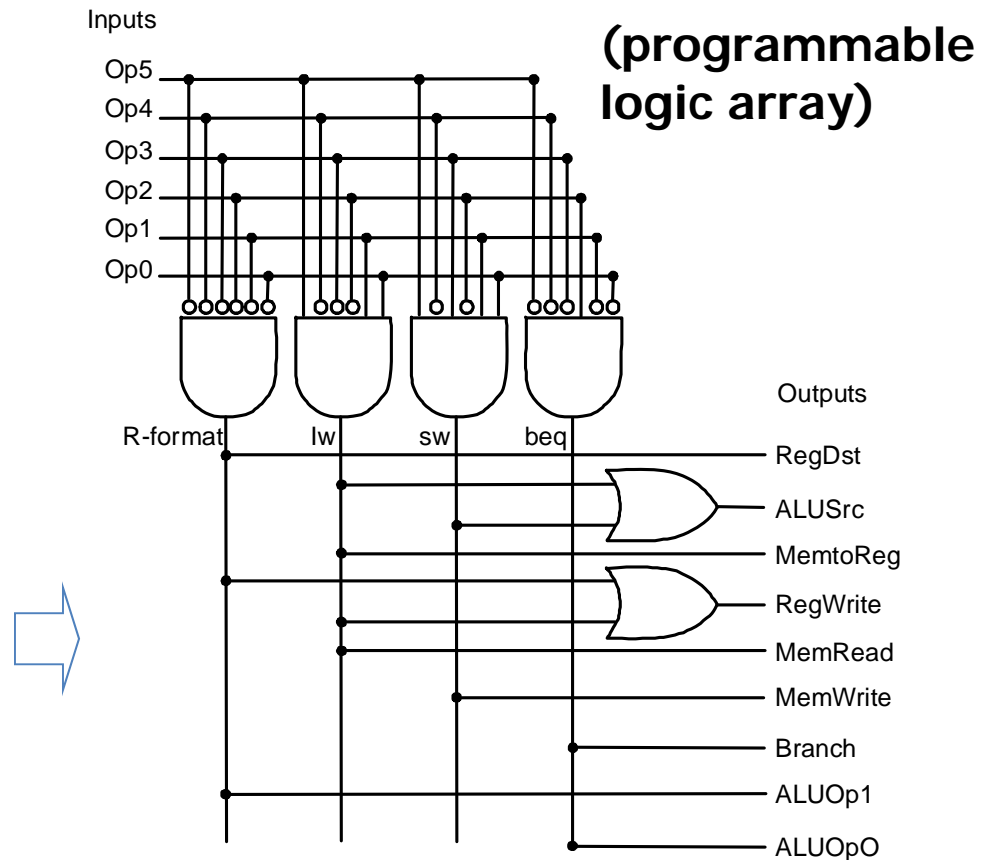


Main control PLA

$$RegDst = \overline{Op5} \cdot \overline{Op4} \cdot \overline{Op3} \cdot \overline{Op2} \cdot \overline{Op1} \cdot \overline{Op0}$$

$$ALUSrc = (Op5 \cdot \overline{Op4} \cdot \overline{Op3} \cdot \overline{Op2} \cdot Op1 \cdot Op0) \text{ or } (Op5 \cdot \overline{Op4} \cdot Op3 \cdot \overline{Op2} \cdot Op1 \cdot Op0)$$



Truth table for main control signals

 



Main Control and ALU Control

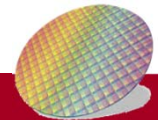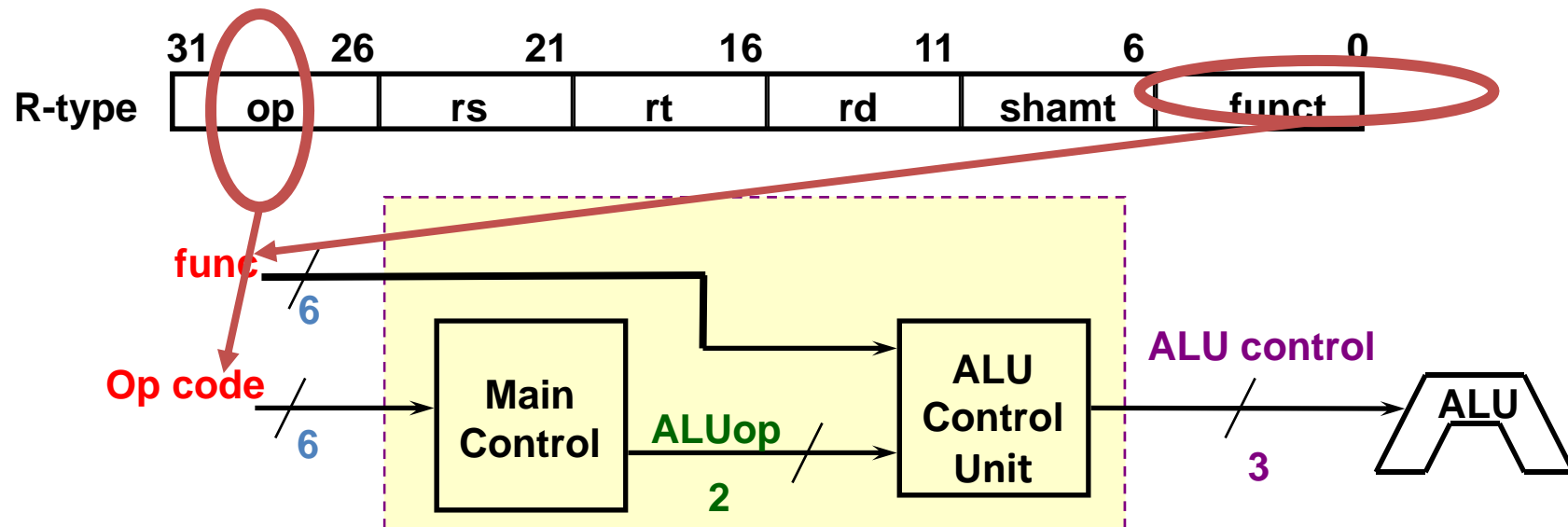
- **Main Control**: Based on opcode, generate RegDst, Branch, MemRead MemtoReg, ALUOp MemWrite, ALUSrc, RegWrite
- **ALU Control**: Based on **2-bit ALUOp** and the **6-bit func field** of instruction, the ALU control unit generates the 3-bit ALU control field



Input		Input		output	
Instruction opcode	ALUOp	Instruction operation	Funct field	Desired ALU action	ALU control input
LW	00	load word	XXXXXX	add	0010
SW	00	store word	XXXXXX	add	0010
Branch equal	01	branch equal	XXXXXX	subtract	0110
R-type	10	add	100000	add	0010
R-type	10	subtract	100010	subtract	0110
R-type	10	AND	100100	AND	0000
R-type	10	OR	100101	OR	0001
R-type	10	set on less than	101010	set on less than	0111

inputs								outputs	
ALUOp		Funct field						Operation	
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	$C_3C_2C_1C_0$	
0	0	X	X	X	X	X	X	0010	(lw/sw) => add
0	1	X	X	X	X	X	X	0110	(beq) => subtract
1	0	X	X	0	0	0	0	0010	(add) => add
1	0	X	X	0	0	1	0	0110	(sub) => subtract
1	0	X	X	0	1	0	0	0000	(and) => and
1	0	X	X	0	1	0	1	0001	(or) => or
1	0	X	X	1	0	1	0	0111	(slt) => slt

$C_3=0, C_2=?, C_1=?, C_0=?$

 


$C_0 = ?$

inputs → outputs

ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	$C_3 C_2 C_1 C_0$
0	0	X	X	X	X	X	X	0010
0	1	X	X	X	X	X	X	0110
1	0	X	X	0	0	0	0	0010
1	0	X	X	0	0	1	0	0110
1	0	X	X	0	1	0	0	0000
1	0	X	X	0	1	0	1	0001
1	0	X	X	1	0	1	0	0111

$C_0 = 1$ at row 6 & row 7, how to identify row 6 and row 7

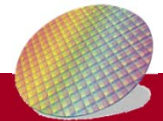$C_0 = (\text{ALOP } 1 \text{ and } F_0) \text{ or } (\text{ALUOP1 and } F_3)$
 $= \text{ALUOP1 and } (F_0 \text{ or } F_3)$



$$C_1 = ?$$

inputs → outputs


ALUOp		Funct field						Operation
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	$C_2 C_2 C_1 C_0$
0	0	X	X	X	X	X	X	0010
0	1	X	X	X	X	X	X	0110
1	0	X	X	0	0	0	0	0010
1	0	X	X	0	0	1	0	0110
1	0	X	X	0	1	0	0	0000
1	0	X	X	0	1	0	1	0001
1	0	X	X	1	0	1	0	0111

C_1 is 1 at row 1, 2, 3, 4 & 7,
How to identify row 1, 2, 3, 4 and 7

$$C_1 = \overline{F_2} \text{ or } \overline{ALUOP1}$$

Row 3 or 4 or 7

Row 1 or 2

 

$C_2 = ?$

inputs outputs

ALUOp		Funct field						Operation $C_3 C_2 C_1 C_0$
ALUOp1	ALUOp0	F5	F4	F3	F2	F1	F0	
0	0	X	X	X	X	X	X	0010
0	1	X	X	X	X	X	X	0110
1	0	X	X	0	0	0	0	0010
1	0	X	X	0	0	1	0	0110
1	0	X	X	0	1	0	0	0000
1	0	X	X	0	1	0	1	0001
1	0	X	X	1	0	1	0	0111

$C_2 = 1$ at row 2, row 4 & row 7

How to identify row 2, row 4, and row 7



$$C_2 = \text{ALUOp0} \text{ or } (\text{ALUOp1} \text{ and } F_1)$$

↑
Row 2

↑
Row 4 & Row 7

$$C_1 = \overline{F_2} \text{ or } \overline{\text{ALUOp1}}$$

 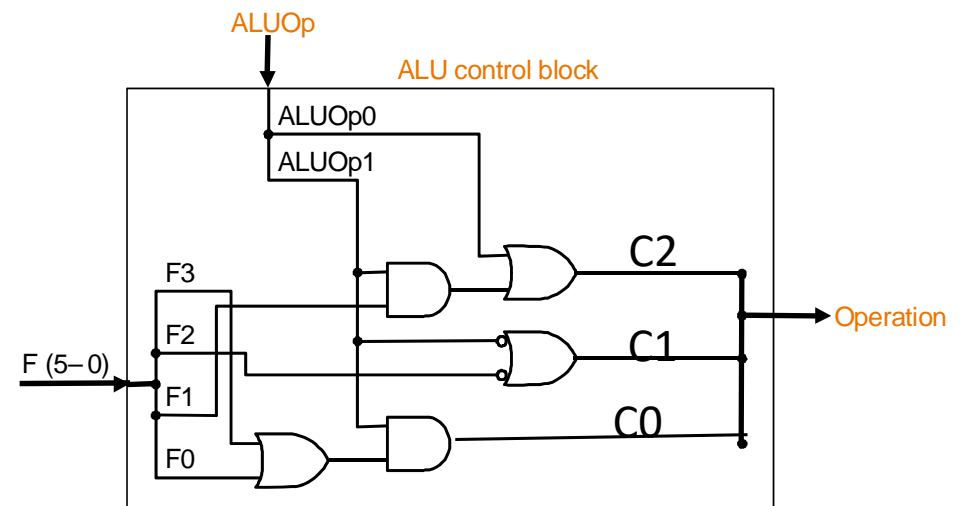
$$C_0 = \text{ALUOp1} \text{ and } (F_0 \text{ or } F_3)$$





Why a SC implementation is not used today

- In single-cycle design, each **clock cycle** must have the same length for every instruction
 - Longest delay determines clock period
- Critical path (longest delay): load instruction
 - Instruction memory → register file → ALU → data memory → register file
- **Performance** is poor because **clock cycle is too long**
 - Violates design principle: Making the common case fast
- We will improve performance by **pipelining**
 - Run multiple instructions simultaneously

 



成功大學

National Cheng Kung University

Backup Slides

