

HW10 CH31 Solutions

- 31.12. IDENTIFY:** Calculate the reactance of the inductor and of the capacitor. Calculate the impedance and use that result to calculate the current amplitude.

SET UP: With no capacitor, $Z = \sqrt{R^2 + X_L^2}$ and $\tan \phi = \frac{X_L}{R}$. $X_L = \omega L$. $I = \frac{V}{Z}$. $V_L = IX_L$ and $V_R = IR$. For an inductor, the voltage leads the current.

EXECUTE: (a) $X_L = \omega L = (250 \text{ rad/s})(0.400 \text{ H}) = 100 \Omega$. $Z = \sqrt{(200 \Omega)^2 + (100 \Omega)^2} = 224 \Omega$.

(b) $I = \frac{V}{Z} = \frac{30.0 \text{ V}}{224 \Omega} = 0.134 \text{ A}$.

(c) $V_R = IR = (0.134 \text{ A})(200 \Omega) = 26.8 \text{ V}$. $V_L = IX_L = (0.134 \text{ A})(100 \Omega) = 13.4 \text{ V}$.

(d) $\tan \phi = \frac{X_L}{R} = \frac{100 \Omega}{200 \Omega}$ and $\phi = +26.6^\circ$. Since ϕ is positive, the source voltage leads the current.

(e) The phasor diagram is sketched in Figure 31.12.

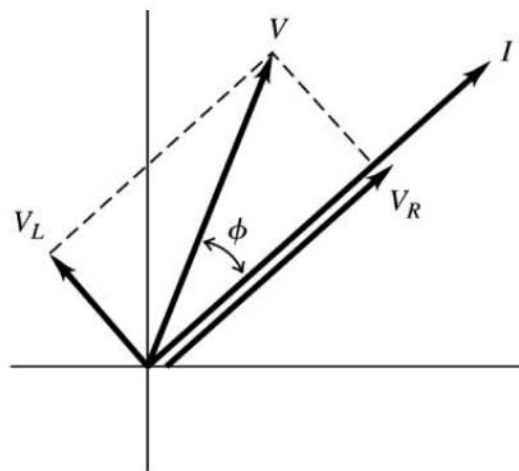


Figure 31.12

- 31.24. IDENTIFY and SET UP:** $P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \cos \phi$. $I_{\text{rms}} = \frac{V_{\text{rms}}}{Z}$. $\cos \phi = \frac{R}{Z}$.

EXECUTE: $I_{\text{rms}} = \frac{73.0 \text{ V}}{119 \Omega} = 0.613 \text{ A}$. $\cos \phi = \frac{76.0 \Omega}{119 \Omega} = 0.639$.

$P_{\text{av}} = (73.0 \text{ V})(0.613 \text{ A})(0.639) = 28.6 \text{ W}$.

- 31.38. IDENTIFY:** We have an L - R - C series ac circuit.

SET UP: $\tan \phi = \frac{X_L - X_C}{R}$, $P_{\text{av}} = \frac{1}{2} I^2 R$, $P_{\text{av}} = \frac{1}{2} IV \cos \phi$.

EXECUTE: (a) We want X_L . Use $\tan \phi = \frac{X_L - X_C}{R}$. $X_L = R \tan \phi + X_C$. Using the numbers gives

$X_L = (300 \Omega) \tan(-53.0^\circ) + 500 \Omega = 102 \Omega$.

(b) We want I . Use $P_{\text{av}} = \frac{1}{2} I^2 R$ and solve for I . $I = \sqrt{2P_{\text{av}}/R}$ gives $I = 0.730 \text{ A}$.

(c) We want V . Use $P_{\text{av}} = \frac{1}{2} IV \cos \phi$ and solve for V . $V = \frac{2P_{\text{av}}}{I \cos \phi} = 364 \text{ V}$.

31.39. IDENTIFY: An L - R - C ac circuit operates at resonance. We know L , C , and V and want to find R .

SET UP: At resonance, $Z = R$ and $\omega = \omega_0 = \frac{1}{\sqrt{LC}}$. $X_C = \frac{1}{\omega C}$, $I = V/Z$.

EXECUTE: $\omega = \frac{1}{\sqrt{LC}} = 626.0 \text{ rad/s}$ $X_C = \frac{1}{\omega C} = \frac{1}{(626 \text{ rad/s})(5.00 \times 10^{-6} \text{ F})} = 319.4 \Omega$.

$I = \frac{V_C}{X_C} = \frac{77.0 \text{ V}}{319.4 \Omega} = 0.2411 \text{ A}$. At resonance $Z = R$, so $I = \frac{V}{R}$. $R = \frac{V}{I} = \frac{57.5 \text{ V}}{0.2411 \text{ A}} = 238 \Omega$.

31.42. IDENTIFY: Use geometry to calculate the self-inductance of the toroidal solenoid. Then find its reactance and use this to find the impedance, and finally the current amplitude, of the circuit.

SET UP: $L = \frac{\mu_0 N^2 A}{2\pi r}$, $X_L = 2\pi fL$, $Z = \sqrt{R^2 + X_L^2}$, and $I = V/Z$.

EXECUTE: $L = \frac{\mu_0 N^2 A}{2\pi r} = (2 \times 10^{-7} \text{ T} \cdot \text{m/A}) \frac{(3000)^2 (0.500 \times 10^{-4} \text{ m}^2)}{9.25 \times 10^{-2} \text{ m}} = 9.73 \times 10^{-4} \text{ H}$.

$X_L = 2\pi fL = (2\pi)(375 \text{ Hz})(9.73 \times 10^{-4} \text{ H}) = 2.292 \Omega$. $Z = \sqrt{R^2 + X_L^2} = 3.618 \Omega$.

$I = \frac{V}{Z} = \frac{23.5 \text{ V}}{3.618 \Omega} = 6.49 \text{ A}$.

31.43. IDENTIFY and SET UP: Source voltage lags current so it must be that $X_C > X_L$.

EXECUTE: (a) We must add an inductor in series with the circuit. When $X_C = X_L$ the power factor has its maximum value of unity, so calculate the additional L needed to raise X_L to equal X_C .

(b) Power factor $\cos \phi$ equals 1 so $\phi = 0$ and $X_C = X_L$. Calculate the present value of $X_C - X_L$ to see how much more X_L is needed: $R = Z \cos \phi = (58.0 \Omega)(0.720) = 41.8 \Omega$

$\tan \phi = \frac{X_L - X_C}{R}$ so $X_L - X_C = R \tan \phi$.

$\cos \phi = 0.720$ gives $\phi = -43.95^\circ$ (ϕ is negative since the voltage lags the current).

Then $X_L - X_C = R \tan \phi = (41.8 \Omega) \tan(-43.95^\circ) = -40.26 \Omega$.

Therefore need to add 40.26Ω of X_L .

$X_L = \omega L = 2\pi fL$ and $L = \frac{X_L}{2\pi f} = \frac{40.26 \Omega}{2\pi(45.0 \text{ Hz})} = 0.142 \text{ H}$, amount of inductance to add.

31.44. IDENTIFY: We are dealing with a transformer as an ac adapter.

SET UP and EXECUTE: (a) Voltage = 19.5 V, current = 6.7 A.

(b) Power = 130 W. $IV = (19.5 \text{ V})(6.7 \text{ A}) = 131 \text{ W}$, so $P = IV$.

(c) Primary: 230 V rms, 200 turns. The full-wave rectifier following the secondary coil maintains a voltage amplitude $V = 19.5 \text{ V}$. We want the number of turns in the secondary. $V_1 = V_{\text{rms}}\sqrt{2}$. The

secondary output should be $V_2 = 19.5 \text{ V}$. $N_2 = \frac{V_2}{V_1} N_1 = \frac{19.5 \text{ V}}{230\sqrt{2} \text{ V}} (200) = 12$ turns.

(d) We want I_1 . $P = IV$ gives $130 \text{ W} = I_1(230 \text{ V})$, so $I_1 = 0.57 \text{ A}$.


(e) Estimate the size: Outside: 5 cm by 5 cm by 1.5 cm. Inside: 3 cm by 3 cm by 1 cm. One coil: 4 cm. 200 coils: 800 cm = 8.0 m.

(f) We want B inside the core. Apply Ampere's law. Use permeability μ instead of μ_0 , where

$\mu = K_m \mu_0$, with K_m being the relative permeability. $\oint \vec{B} \cdot d\vec{l} = K_m \mu_0 I_{\text{encl}}$. Use a rectangular path with one side of length $l = 3 \text{ cm}$ inside the core enclosing all the loops. $Bl = K \mu_0 N_1 I_{\text{encl}}$.

$B = K \mu_0 N_1 I_{\text{encl}} / l = (5000) \mu_0 (200)(0.57 \text{ A}) / (0.030 \text{ m}) = 24 \text{ T}$.

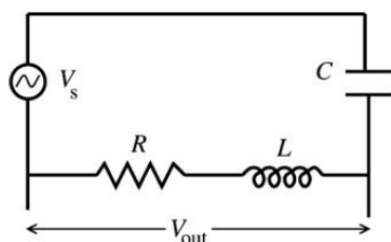- 31.47. IDENTIFY and SET UP:** Express Z and I in terms of ω , L , C , and R . The voltages across the resistor and the inductor are 90° out of phase, so $V_{\text{out}} = \sqrt{V_R^2 + V_L^2}$.
EXECUTE: The circuit is sketched in Figure 31.47.



$$X_L = \omega L, X_C = \frac{1}{\omega C}$$

$$Z = \sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}$$

$$I = \frac{V_s}{Z} = \frac{V_s}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

Figure 31.47

$$V_{\text{out}} = I\sqrt{R^2 + X_L^2} = I\sqrt{R^2 + \omega^2 L^2} = V_s \frac{\sqrt{R^2 + \omega^2 L^2}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

$$\frac{V_{\text{out}}}{V_s} = \frac{\sqrt{R^2 + \omega^2 L^2}}{\sqrt{R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2}}$$

ω small:

$$\text{As } \omega \text{ gets small, } R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \rightarrow \frac{1}{\omega^2 C^2}, R^2 + \omega^2 L^2 \rightarrow R^2.$$

$$\text{Therefore, } \frac{V_{\text{out}}}{V_s} \rightarrow \sqrt{\frac{R^2}{(1/\omega^2 C^2)}} = \omega RC \text{ as } \omega \text{ becomes small.}$$

ω large:

$$\text{As } \omega \text{ gets large, } R^2 + \left(\omega L - \frac{1}{\omega C}\right)^2 \rightarrow R^2 + \omega^2 L^2 \rightarrow \omega^2 L^2, R^2 + \omega^2 L^2 \rightarrow \omega^2 L^2.$$

$$\text{Therefore, } \frac{V_{\text{out}}}{V_s} \rightarrow \sqrt{\frac{\omega^2 L^2}{\omega^2 L^2}} = 1 \text{ as } \omega \text{ becomes large.}$$

- 31.48. IDENTIFY:** $V = V_C = IX_C$. $I = V/Z$.

$$\text{SET UP: } X_L = \omega L, X_C = \frac{1}{\omega C}.$$

$$\text{EXECUTE: } V_{\text{out}} = V_C = \frac{I}{\omega C} \Rightarrow \frac{V_{\text{out}}}{V_s} = \frac{1}{\omega C \sqrt{R^2 + (\omega L - 1/\omega C)^2}}.$$

$$\text{If } \omega \text{ is large: } \frac{V_{\text{out}}}{V_s} = \frac{1}{\omega C \sqrt{R^2 + (\omega L - 1/\omega C)^2}} \approx \frac{1}{\omega C \sqrt{(\omega L)^2}} = \frac{1}{(LC)\omega^2}.$$

$$\text{If } \omega \text{ is small: } \frac{V_{\text{out}}}{V_s} \approx \frac{1}{\omega C \sqrt{(1/\omega C)^2}} = \frac{\omega C}{\omega C} = 1.$$

31.51. IDENTIFY: We know R , X_C , and ϕ so $\tan\phi = \frac{X_L - X_C}{R}$ tells us X_L . Use $P_{\text{av}} = I_{\text{rms}}^2 R$ to calculate

I_{rms} . Then calculate Z and use $V_{\text{rms}} = I_{\text{rms}} Z$ to calculate V_{rms} for the source.

SET UP: Source voltage lags current so $\phi = -54.0^\circ$. $X_C = 350\ \Omega$, $R = 180\ \Omega$, $P_{\text{av}} = 140\ \text{W}$.

EXECUTE: (a) $\tan\phi = \frac{X_L - X_C}{R}$.

$$X_L = R \tan\phi + X_C = (180\ \Omega) \tan(-54.0^\circ) + 350\ \Omega = -248\ \Omega + 350\ \Omega = 102\ \Omega.$$

$$(b) P_{\text{av}} = V_{\text{rms}} I_{\text{rms}} \cos\phi = I_{\text{rms}}^2 R \text{ (Exercise 31.22). } I_{\text{rms}} = \sqrt{\frac{P_{\text{av}}}{R}} = \sqrt{\frac{140\ \text{W}}{180\ \Omega}} = 0.882\ \text{A}.$$

$$(c) Z = \sqrt{R^2 + (X_L - X_C)^2} = \sqrt{(180\ \Omega)^2 + (102\ \Omega - 350\ \Omega)^2} = 306\ \Omega.$$

$$V_{\text{rms}} = I_{\text{rms}} Z = (0.882\ \text{A})(306\ \Omega) = 270\ \text{V}.$$

31.54. IDENTIFY: At any instant of time the same rules apply to the parallel ac circuit as to the parallel dc circuit: the voltages are the same and the currents add.

SET UP: For a resistor the current and voltage in phase. For an inductor the voltage leads the current by 90° and for a capacitor the voltage lags the current by 90° .

EXECUTE: (a) The parallel L - R - C circuit must have equal potential drops over the capacitor, inductor and resistor, so $v_R = v_L = v_C = v$. Also, the sum of currents entering any junction must equal the current leaving the junction. Therefore, the sum of the currents in the branches must equal the current through the source: $i = i_R + i_L + i_C$.

(b) $i_R = \frac{v}{R}$ is always in phase with the voltage. $i_L = \frac{v}{\omega L}$ lags the voltage by 90° , and $i_C = v\omega C$ leads the voltage by 90° . The phasor diagram is sketched in Figure 31.54.

$$(c) \text{ From the diagram, } I^2 = I_R^2 + (I_C - I_L)^2 = \left(\frac{V}{R}\right)^2 + \left(V\omega C - \frac{V}{\omega L}\right)^2.$$

$$(d) \text{ From part (c): } I = V \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}. \text{ But } I = \frac{V}{Z}, \text{ so } \frac{1}{Z} = \sqrt{\frac{1}{R^2} + \left(\omega C - \frac{1}{\omega L}\right)^2}.$$

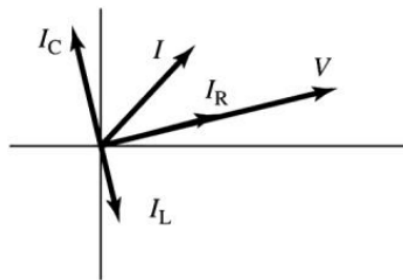


Figure 31.54

31.65. IDENTIFY: We have an L - R ac circuit.

SET UP: $v_{\text{in}} = V_{\text{in}} \cos \omega t$, $G = (20 \text{ dB}) \ln(V_{\text{out}}/V_{\text{in}})$, $I = V_{\text{in}}/Z$, $Z = \sqrt{R^2 + (\omega L)^2}$, $\phi = \arctan\left(\frac{\omega L}{R}\right)$.

EXECUTE: (a) We want the current. $I = \frac{V_{\text{in}}}{Z} = \frac{V_{\text{in}}}{\sqrt{R^2 + (\omega L)^2}}$.

(b) We want ϕ . $\phi = \arctan\left(\frac{\omega L}{R}\right)$.

(c) We want $V_{\text{out}}/V_{\text{in}}$. $\frac{V_{\text{out}}}{V_{\text{in}}} = \frac{V_L}{V_{\text{in}}} = \frac{IX_L}{V_{\text{in}}} = \frac{V_{\text{in}}}{\sqrt{R^2 + (\omega L)^2}} \cdot \omega L = \frac{\omega L}{\sqrt{R^2 + (\omega L)^2}} = \frac{1}{\sqrt{1 + (R/\omega L)^2}}$.

(d) We want f so $G = -3.0 \text{ dB}$. Use $G = (20 \text{ dB}) \ln(V_{\text{out}}/V_{\text{in}})$. $-3.0 \text{ dB} = (20 \text{ dB}) \ln(V_{\text{out}}/V_{\text{in}})$. $-3.0 / 20 = \ln(V_{\text{out}}/V_{\text{in}})$. Write this result in terms of exponents and use the result from (c).

$10^{-3.0/20} = 0.708 = \frac{V_{\text{out}}}{V_{\text{in}}} = \frac{1}{\sqrt{1 + (R/\omega L)^2}}$. Use $\omega = 2\pi f$ and solve for f , giving $f = \frac{R}{2.00\pi L}$.

(e) We want L . Solve the result in (d) when $f = 10.0 \text{ kHz}$ and $R = 100 \Omega$, giving $L = 1.6 \text{ mH}$.